



Wideband pulse amplifier for the integrated camera of the Cherenkov Telescope Array

E. Delagnes^a, A. Sanuy^b, D. Gascón^b

on behalf of the **NECTAr** collaboration

I r f u

cea

saclay



Irfu /CEA/Saclay ^a

LPNHE / Paris

LPTA / Montpellier

ICC / Universitat Barcelona (ICC-UB) ^b

LPNHE
Laboratoire de
physique nucléaire
et des hautes énergies



Institut de Ciències del Cosmos

I. Introduction


II. Basic building blocks

III. First prototype: ACTA


IV. Second prototype: ACTA3

V. Summary

I. Introduction: Cherenkov telescopes


 


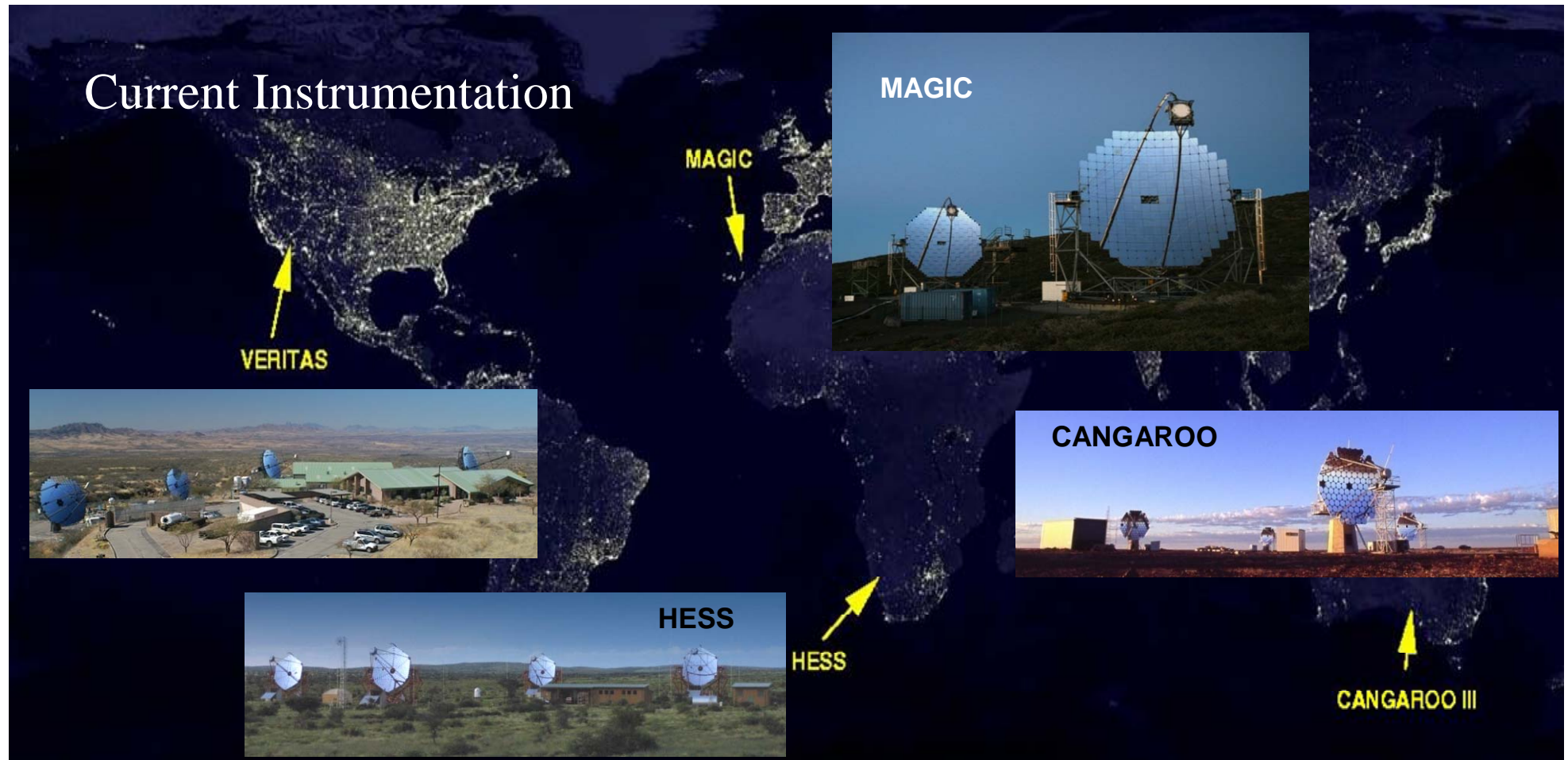I. Introduction: the Cherenkov Telescope Array (CTA) observatory



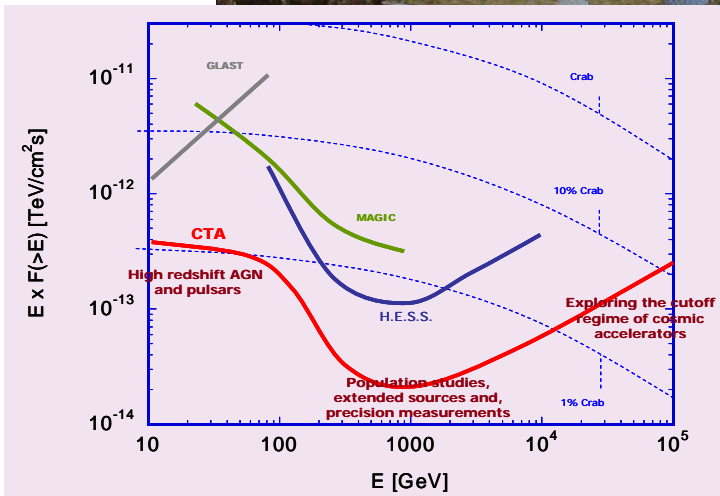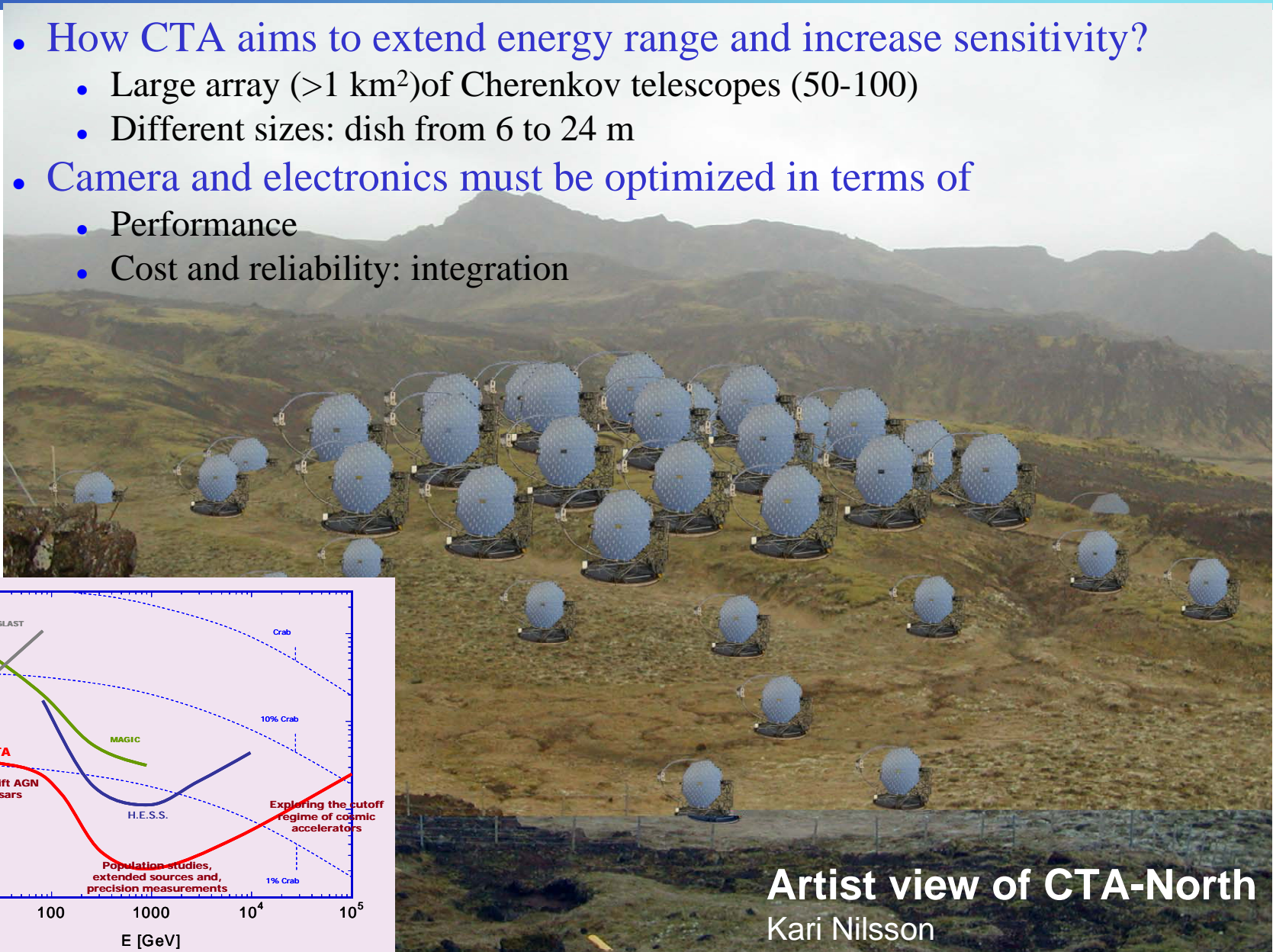I. Introduction: the Cherenkov Telescope Array (CTA) observatory


- How CTA aims to extend energy range and increase sensitivity?
 - Large array (>1 km²) of Cherenkov telescopes (50-100)
 - Different sizes: dish from 6 to 24 m
- Camera and electronics must be optimized in terms of
 - Performance
 - Cost and reliability: integration



Artist view of CTA-North
Kari Nilsson


 
I. Introduction: the camera

- **Front end electronics:**
 - Pixel: fast photosensors
 - High QE PMTs // SiPM
 - Modularity: cluster of 7/8 pixels
 - Front end electronics in the camera
 - Digitization & trigger
- **Huge dynamic range: 16 bits**
 - Signals up to 6 Kphe
 - Single phe resolution for calibration:
 - Series noise $< 3 \text{ nV}/\sqrt{\text{Hz}}$



HESS cluster

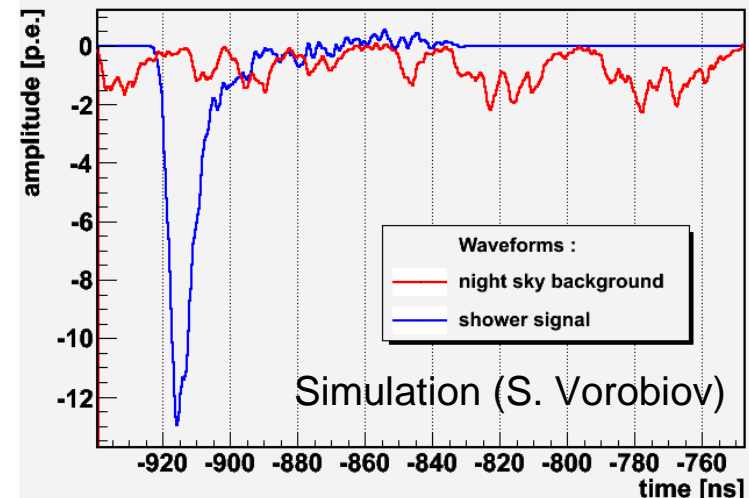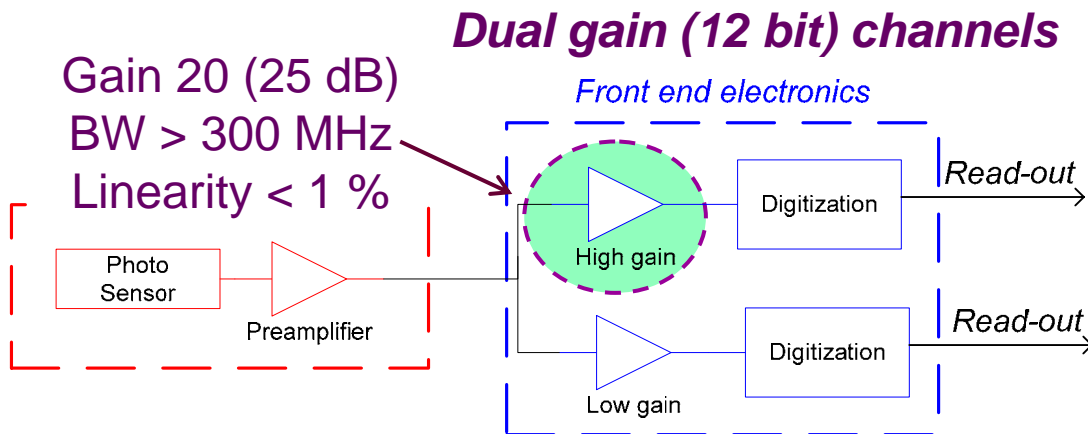
- **High BW (>300 MHz):**
 - Night Sky Background:
 - Up to 100 MHz
 - Minimize integration time



 I. Introduction: readout electronics


• Analogue memory + slow digitization

- Sample and hold in a capacitor array
 - High speed: up to 3 GS/s (> 300 MHz analogue BW)
- Slow digitization for selected events
 - Trigger system
- Custom ASICs developed in the community
 - Domino Ring Sampler (DRS) by PSI
 - For CTA: **DRAGON** project
 - Sampling Analogue Memory (SAM) by Irfu
 - For CTA: **NECTAr** project



• Flash ADCs

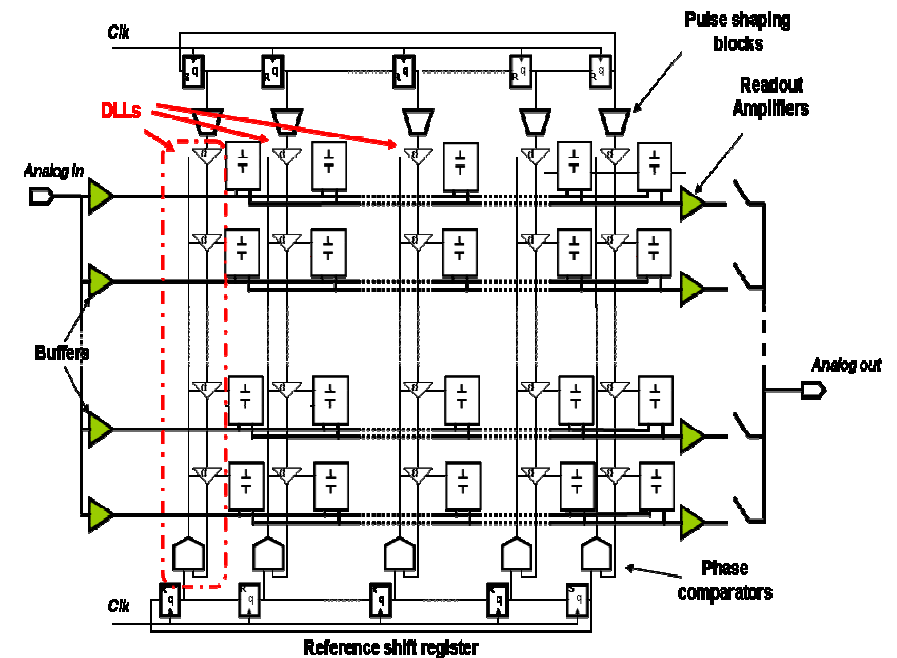
- Commercial component
- Limited to 500 MS/s
 - High Cost and power consumption
 - For CTA: FlashCam collaboration
 - No trigger needed






 I. Introduction: NECTAr (Irfu/Saclay, LPNHE, LPTA and ICC-UB)

- From HESS chip (SAM: only analogue memory) to a single chip integrating full acquisition channel:
 - NECTAr chip: *COST & RELIABILITY*



E. Delagnes

 


FE board HESS-2

Chip 2: Integrated local trigger:

- 8 or 16 fast comparators.
- Coincidences in < 1 ns

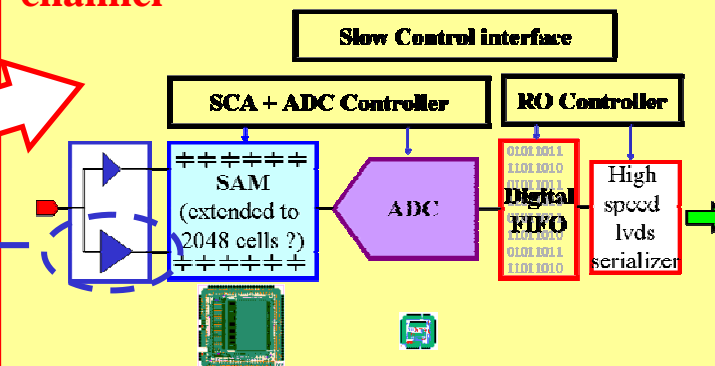Chip 1 = full integrated acquisition channel



- Input signal amplif. (2 gains),
- Analog memory (depth adapted to CTA trigger latency)
- ADC Wilky (already exists),
- FIFO
- Sérialyzer ~300Mb/s.




I. Introduction: NECTAr (Irfu/Saclay, LPNHE, LPTA and ICC-UB)

- From HESS chip (SAM: only analogue memory) to a single chip integrating full acquisition channel:

Accuracy	1-3 %
Bandwidth	400 MHz
Output range	1.5 to 2 Vpp
Gain	20
Temp. Coeff.	< 0.05 %/K
Power	< 50 mW
Slew rate	1500 V/ μ s
Series noise	< 3 nV/ $\sqrt{\text{Hz}}$
Fully differential	

AMS CMOS 0.35 μ m

- SAM technology

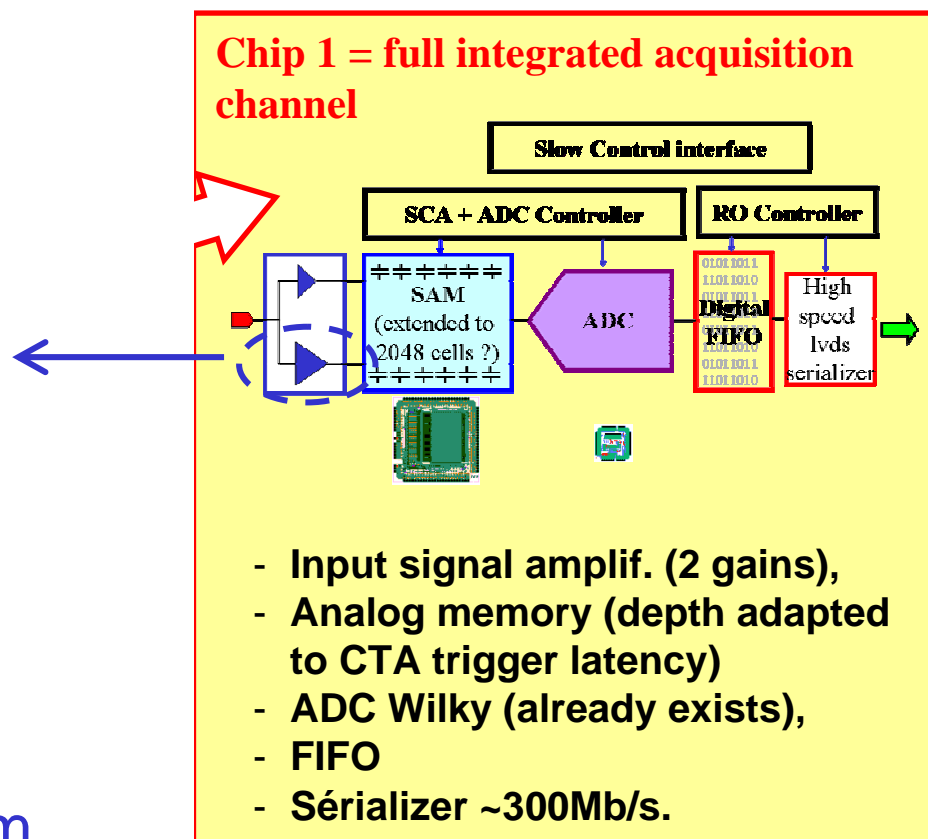

I. Introduction

II. The circuit


III. First prototype: ACTA

IV. Second prototype: ACTA3

V. Summary


II. The circuit: classical topologies for linear voltage amplifiers

• Global feedback

 

- Good linearity
- OpAmp with GBW > 8 GHz !!
 - Reported: < 1 GHz in 0.35 μm
 - Very difficult even with VDSM


• Bipolar style “open loop”

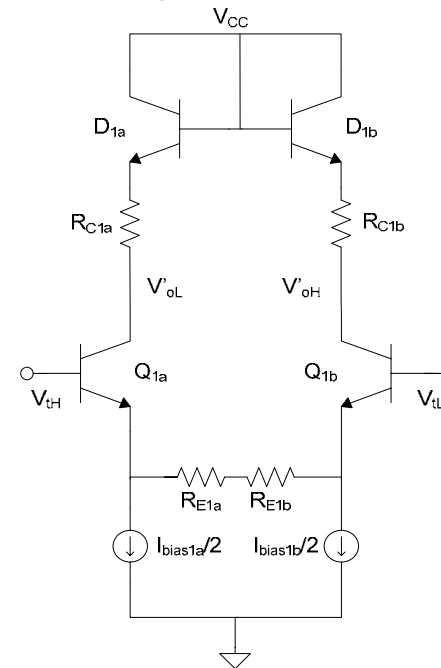


- Limited linearity
- Dynamic of 2 V impossible @ 3.3 V

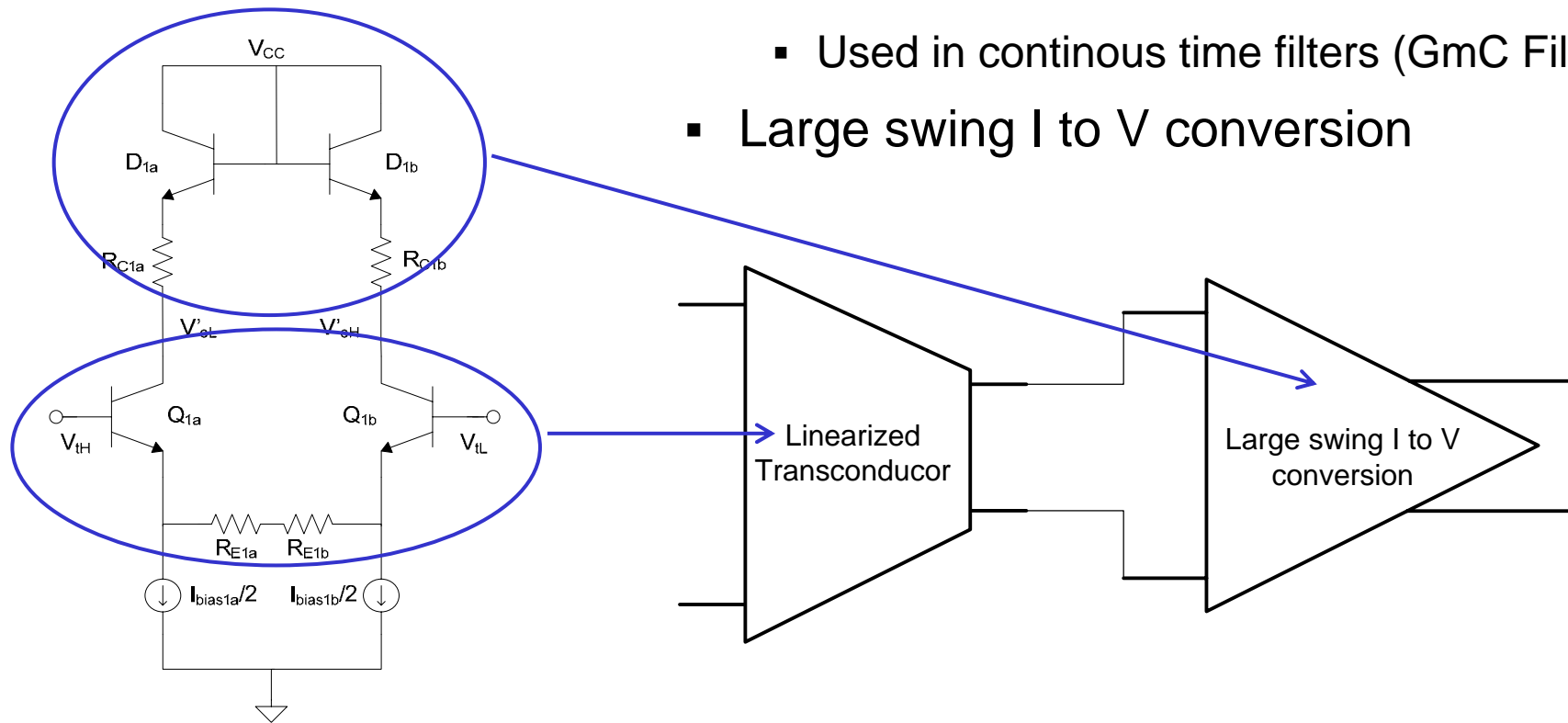II. The circuit: new approach

- Dedicated CMOS topologies
- Local feedback
 - Linearized HF CMOS transconductor
 - Used in continuous time filters (GmC Filters)
 - Large swing I to V conversion




II. The circuit: HF transconductors

 

- Classical solution with global feedback looks impossible
 - Max. OpAmp GBW 500 MHz to 1 GHz (need > 5GHz)
- HF transconductors with linearisation by local feedback

	Lin. Err. [%]	BW [MHz]	Noise [nV / $\sqrt{\text{Hz}}$]	Bias current [mA]	Comments
Simple dif. Pair	2	1000	2.2	4.5	W/L limited by linearity
Dif. Pair with degeneration	1	1000	2.7	4.5	Limited range
Cross coupled (XC) mismatched	3	2000	5.7	4.5	Low Gm/Ibias
XC with offset Wang-Guggenbuhl	0.5	850	3.2	8	High consumption
XC with bias offset Szczepanski	0.5	1000	2.5	4.5	Accurate control of Gm with bias offset voltage
Adaptative Nedungadi-Viswanathan	Small range	1000	2.5	7.5	Small linear range even for high bias current

 II. The circuit: bias-offset cross coupled differential pair



- Completely linear

$$I_{oD} = KV_b V_{iD}$$

$$K = \frac{1}{2} \mu C_{ox} \frac{W}{L}$$

- First order:


- Linear using square law MOS: saturation

$$\longrightarrow |V_{in}| \leq \sqrt{\frac{I_{bias}}{K} - \frac{3}{4} V_b^2} - \frac{V_b}{2}$$

- Tuneable gain

- Second order effects on linearity

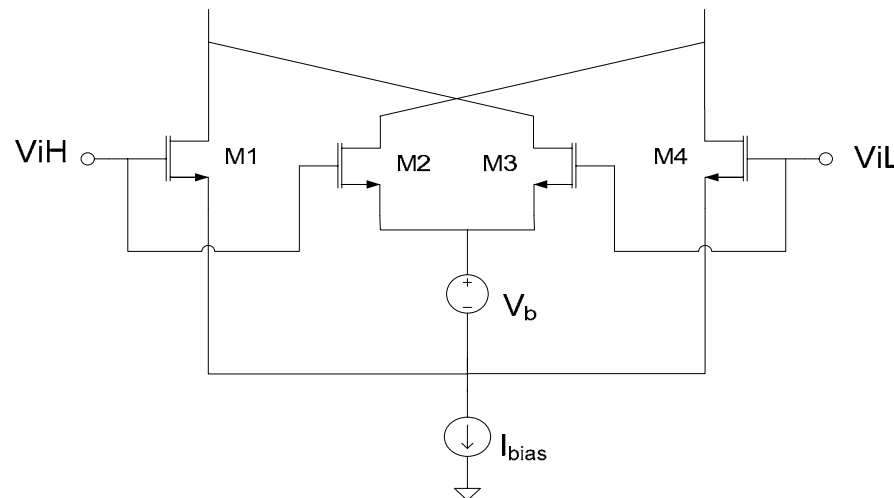- Channel length modulation \longrightarrow Control V_{DS} variations: next slides
 - Mismatch \longrightarrow Large WL and common centroid
 - Mobility reduction \longrightarrow Scaling M1-4 vs M2-3 (for a given G_m)
 - Body effect \longrightarrow Cannot use PMOS (large K needed)




GBW & Noise



$$G_m = KV_b \geq 5 \text{ mS}$$

- $L \Rightarrow$ minimal (0.35 μm)
 - Maximize GBW
 - V_{ds} must be stable!
- W about 150 μm
 - GBW and noise
 - Saturation


II. The circuit: floating voltage source

 

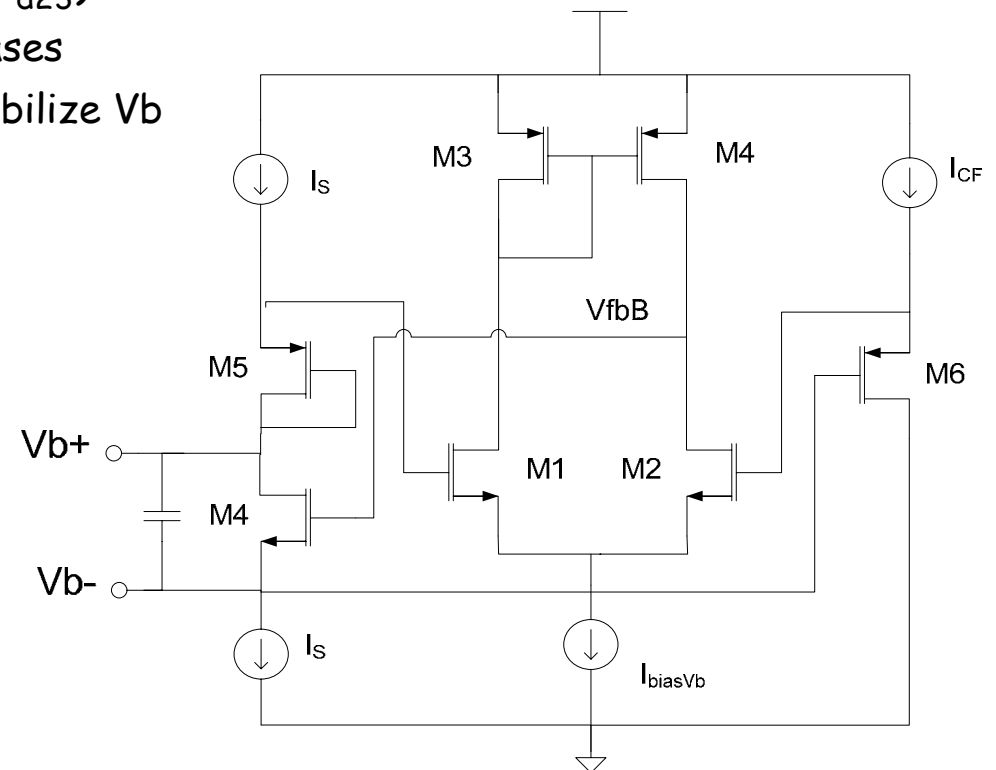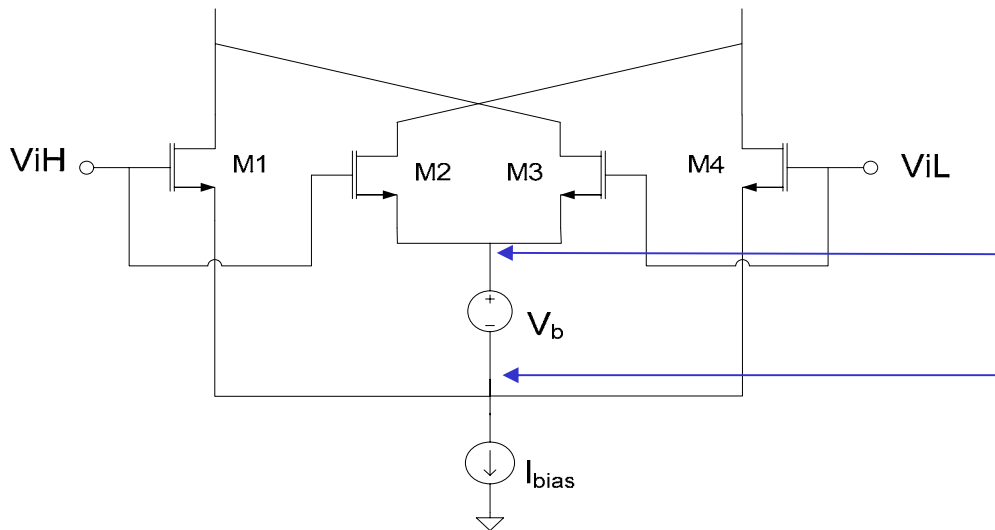- A floating voltage source is needed (V_b)
- Bias voltage is offset in V_{gs} of two matched PMOS
 - Offset by different drain currents: I_b (fixed) vs I_{cf} (control)
- In closed loop (negative feedback) to decrease r_{out} of V_b
 - Must be independent of $M2/M3$ (I_{d23}) drain current
 - V_{gs} of MP3 increases if I_{d23} increases
 - Error amplifier changes V_{fbB} to stabilize V_b



 
II. The circuit: folded regulated cascode common gate



- Regulated cascode

- Folded: large voltage swing
- Low input impedance
 - BW
 - Linearity
 - » Channel length modulation in input pair

R_C	$< 1.5 \text{ K}\Omega$	BW
G_m	$> 5 \text{ mS}$	Gain (noise)
I_b	$4 - 6 \text{ mA}$	Linearity
V_b	$< 300 \text{ mV}$	Range

 

I. Introduction

II. The circuit


III. First prototype: ACTA

IV. Second prototype: ACTA3


V. Summary

III. First prototype: ACTA chip


- First prototype (ACTA chip)
- Voltage buffer
 - Source follower

 

 
CMOS 0.35um
AMS 3 mm²
Submitted: July 20th 2009
Received: October 26th



- Gain tunable from 5 to 20

 


Results of the first prototype

 


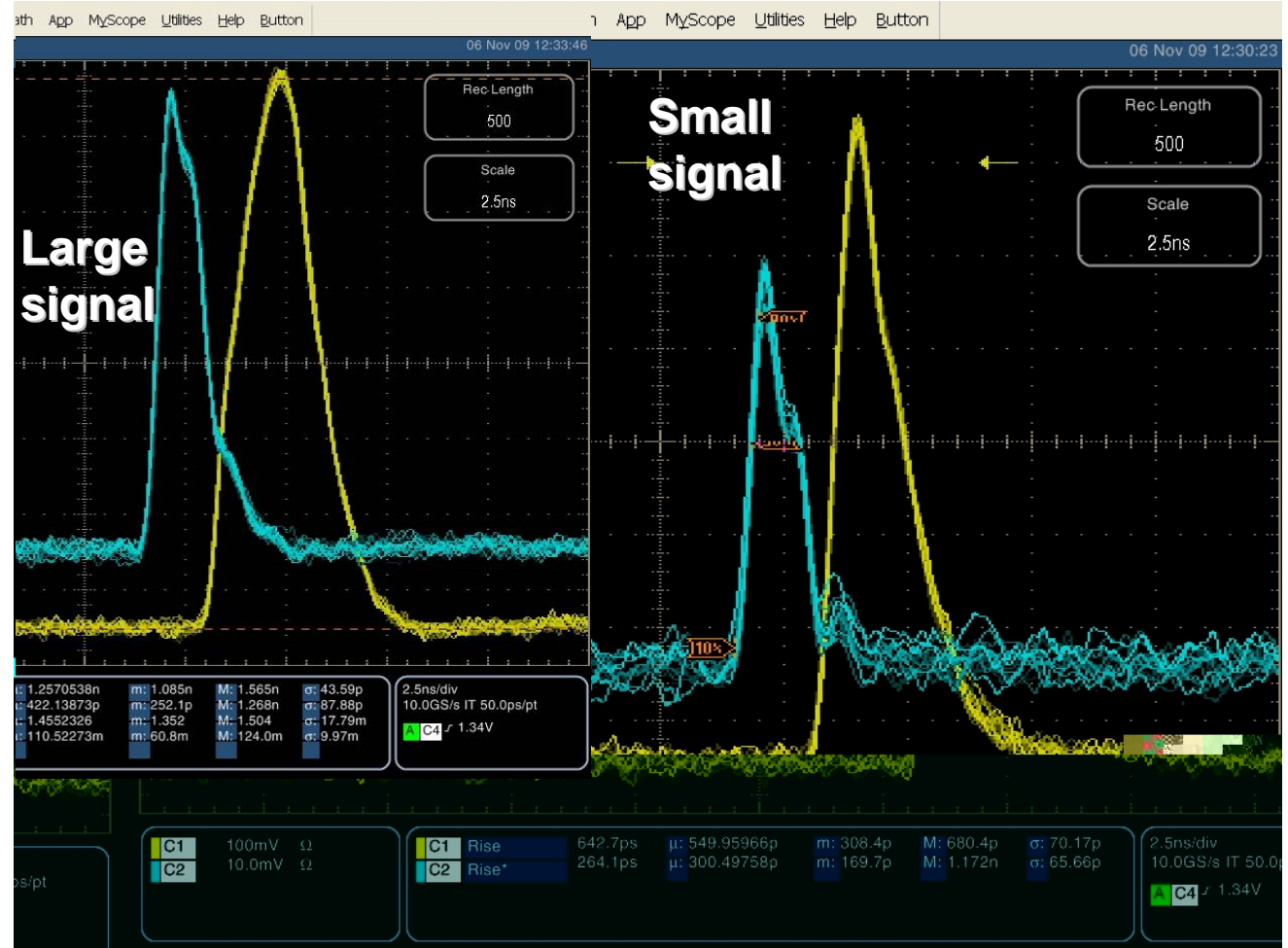
III. First prototype: ACTA chip

- Working
 - No ringing
 - Gain: 5 to 20
- Fast input pulse
 - Rise: 300 ps
- Output pulse
 - Rise time:
 - Small signal ($< 1V$)
 - 550 ps
 - High signal ($> 1V$)
 - 1.2 ns



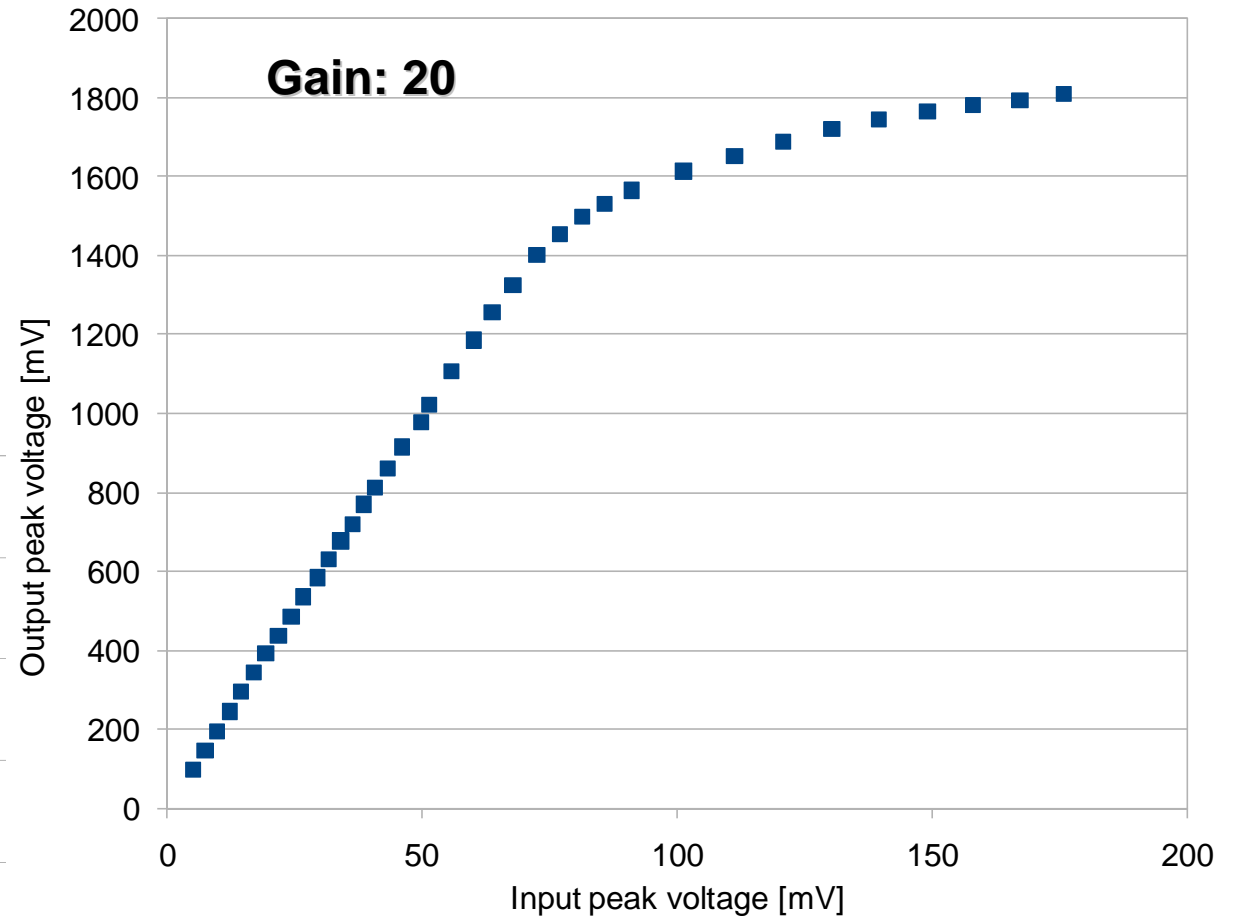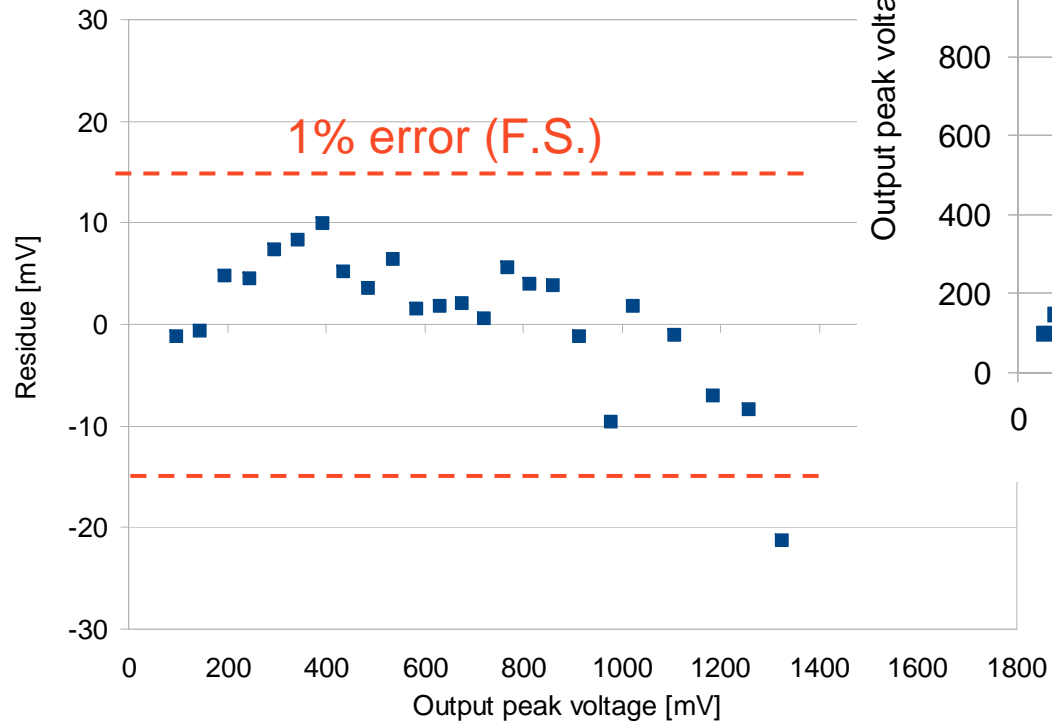
III. ACTA chip: linearity

- Gain:
 - Tunnable
- Linear range
 - About 1.4 V



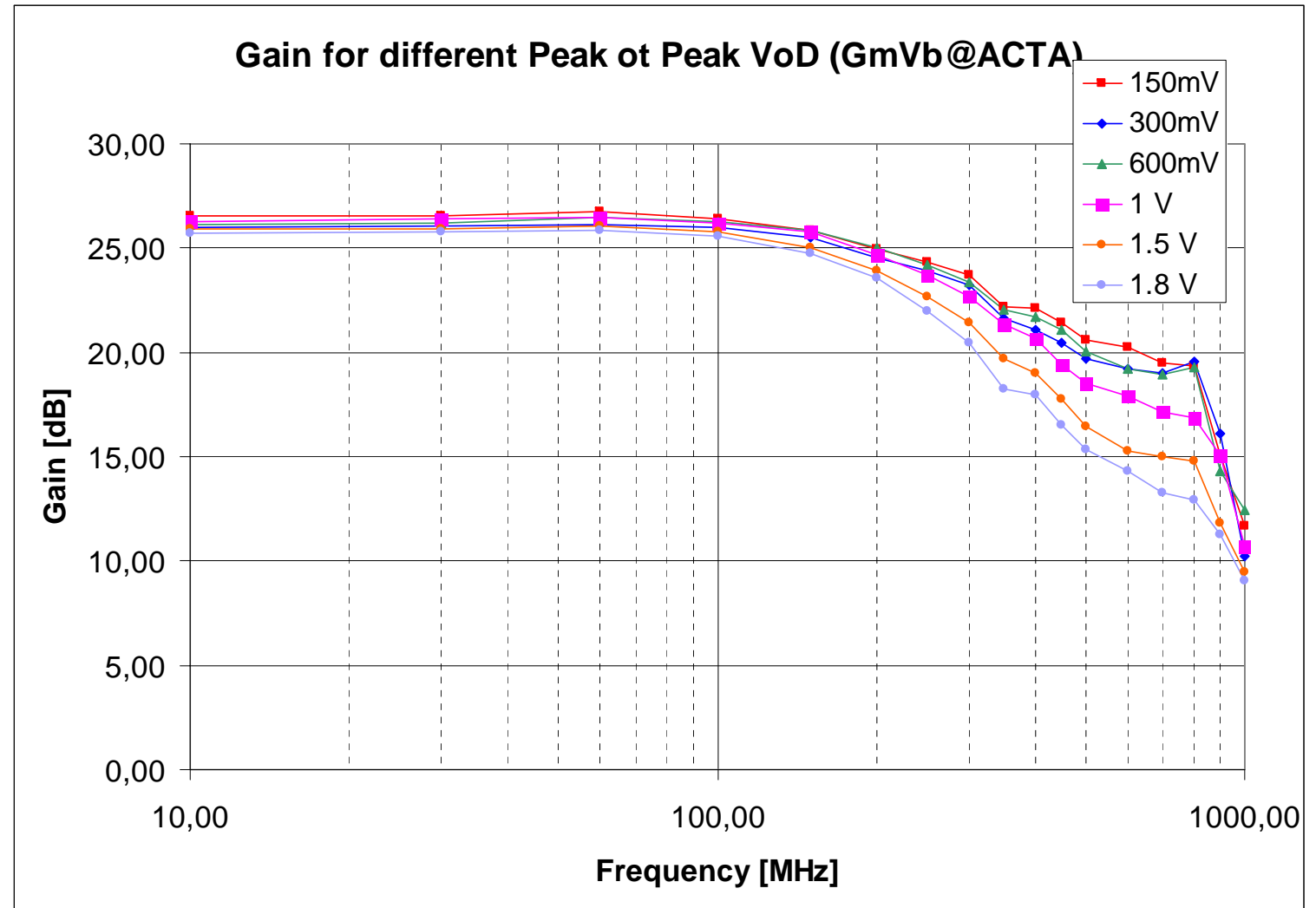III. ACTA chip: frequency response

- Cut-off (3dB)
 - About 300 MHz
- Non-linearity
 - For $V_{oD} > 1$ Vpp
- C_L about 5pF
 - < 1 pF when driving on-chip analogue memory input buffers





Outlook

- I. Introduction
- II. The circuit
- III. First prototype: ACTA
- IV. Second prototype: ACTA3**
- V. Summary

 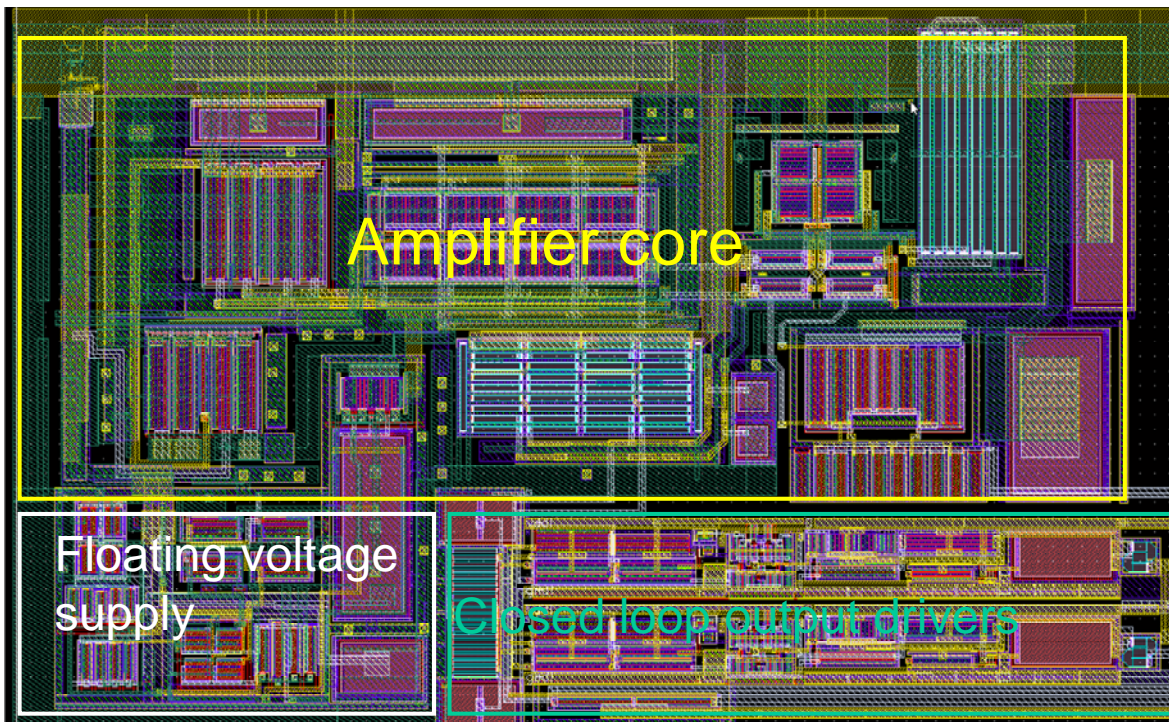IV. Second prototype: ACTA3

- Closed loop buffer to replace source followers
 - Better linearity
 - Lower power consumption: class AB amplifier
 - Good slew rate with low quiescent current !
 - New version of a SAM OpAmp
 - Developed in collaboration with Irfu/Saclay



- Closed loop buffer: Miller OpAmp
- Double current boost of output nMOS
 - Linear boost
 - Class B with nonlinear ctrl: off @ small signal
 - x6 boost with 750 uA (DC) total bias current
- Series resistor at the output (R_d) for C_L pole compensation
 - Limits BW



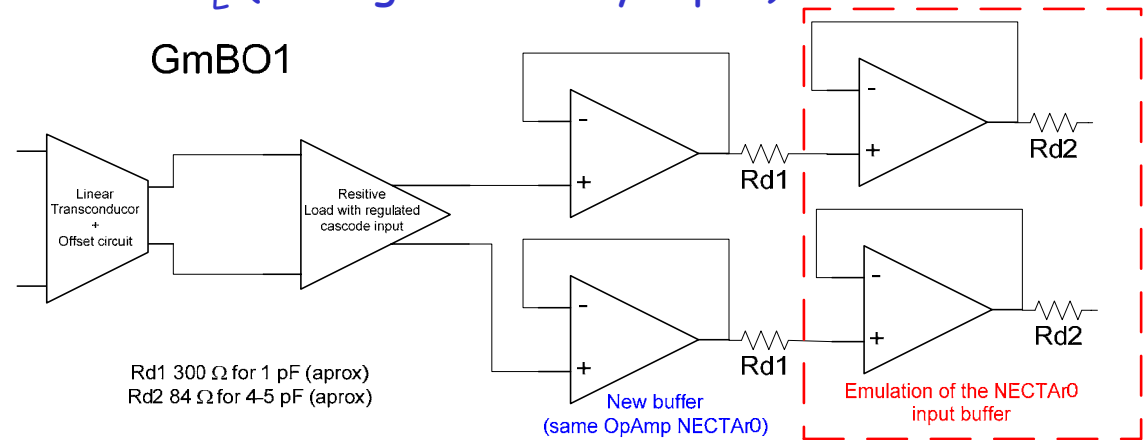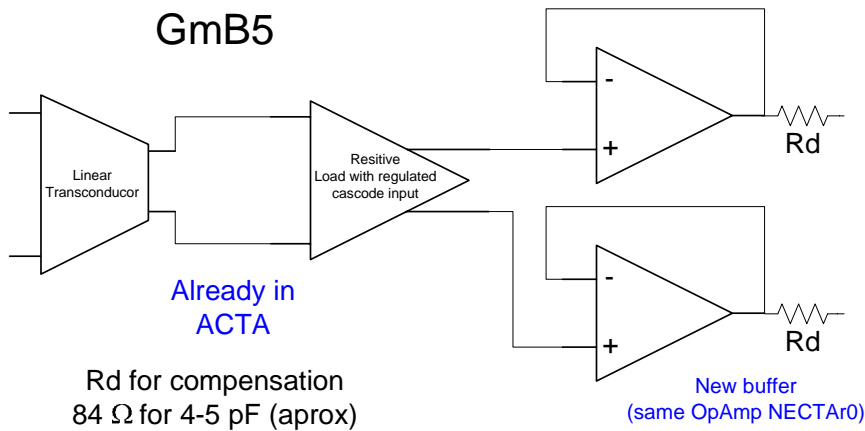IV. ACTA3: 4 configurations



- Same gain block as in ACTA
- Not tested, only to "debug"

- As GmBO5 but the amplifier (R_{d1}) adjusted to drive a smaller C_L (analogue memory input)




- As GmB5 but gain stage is modified to generate the DC offset required by ADC

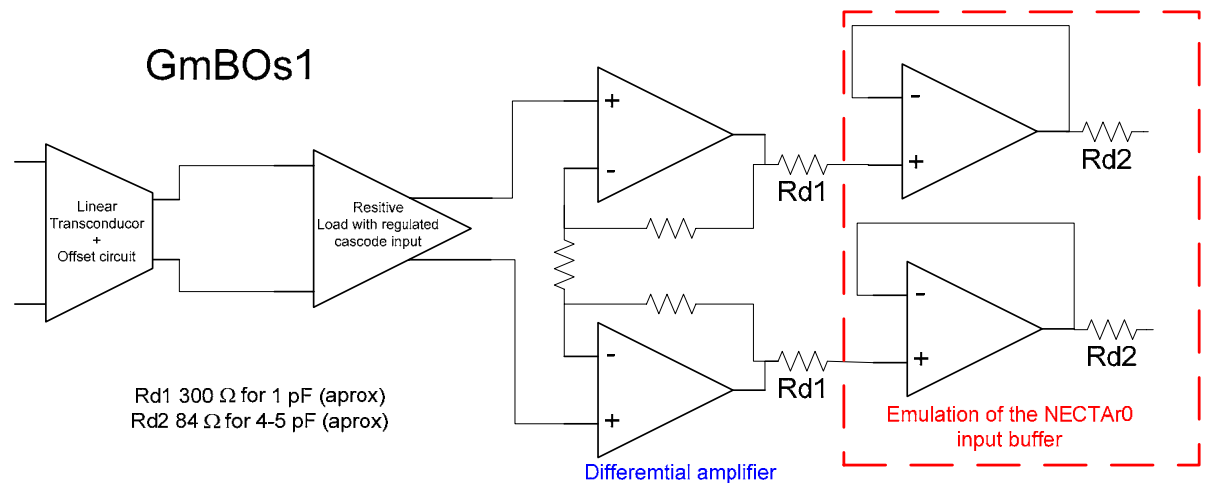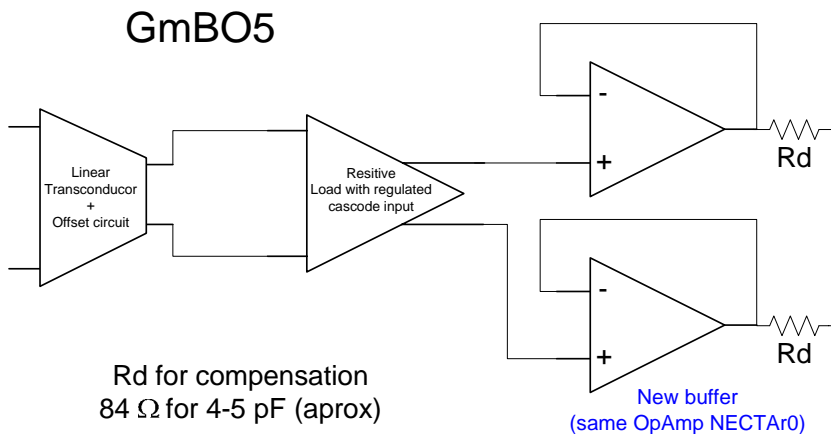- As GmBO1 but buffer replaced by diff. amp:
 - Subtract common mode signals (CMRR, PSRR)



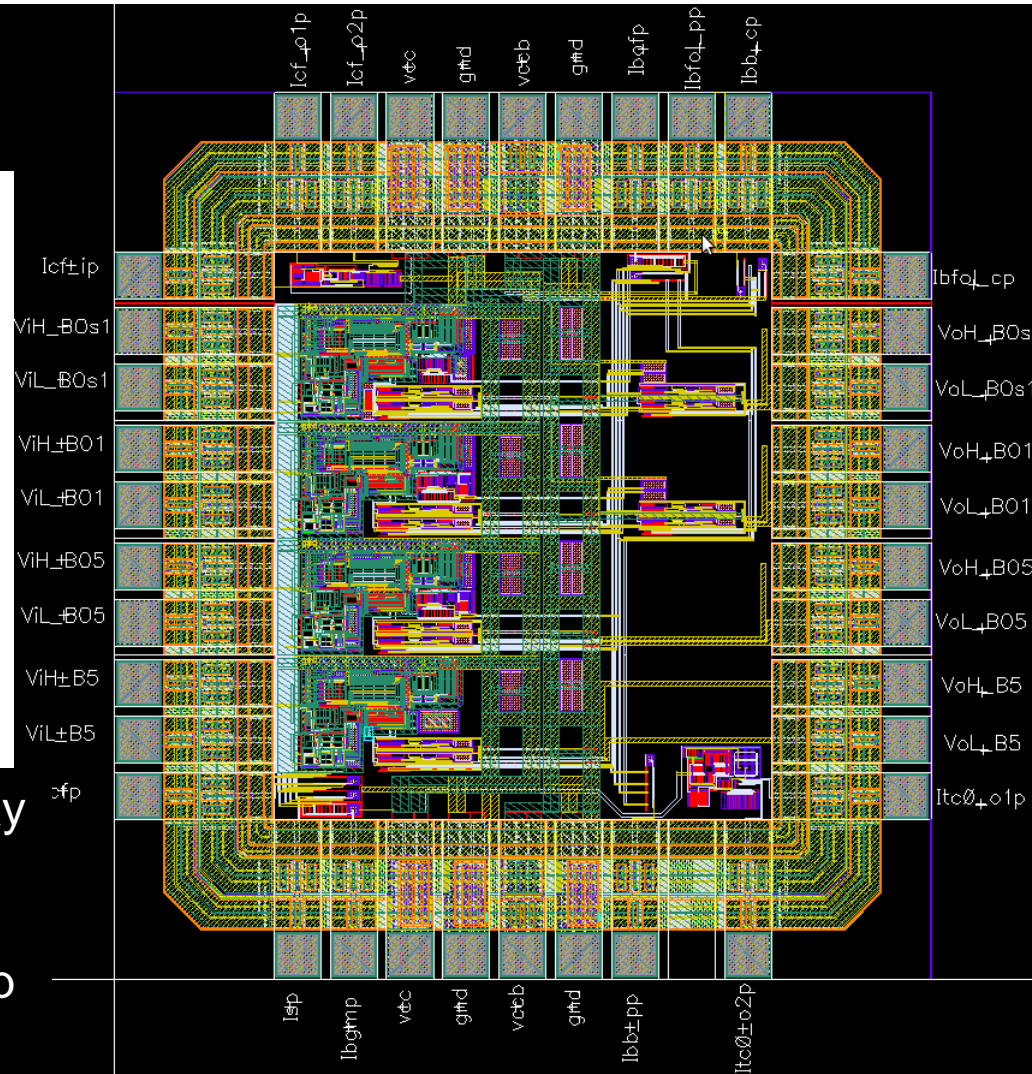IV. ACTA3: 4 configurations


CMOS 0.35um
 AMS 3 mm²
 Submitted: April 2010
 Received: end July 2010



Produced in Irfu/Saclay
 engineering run with
 first prototype of the
 analogue memory chip
 for CTA: NETCAR0

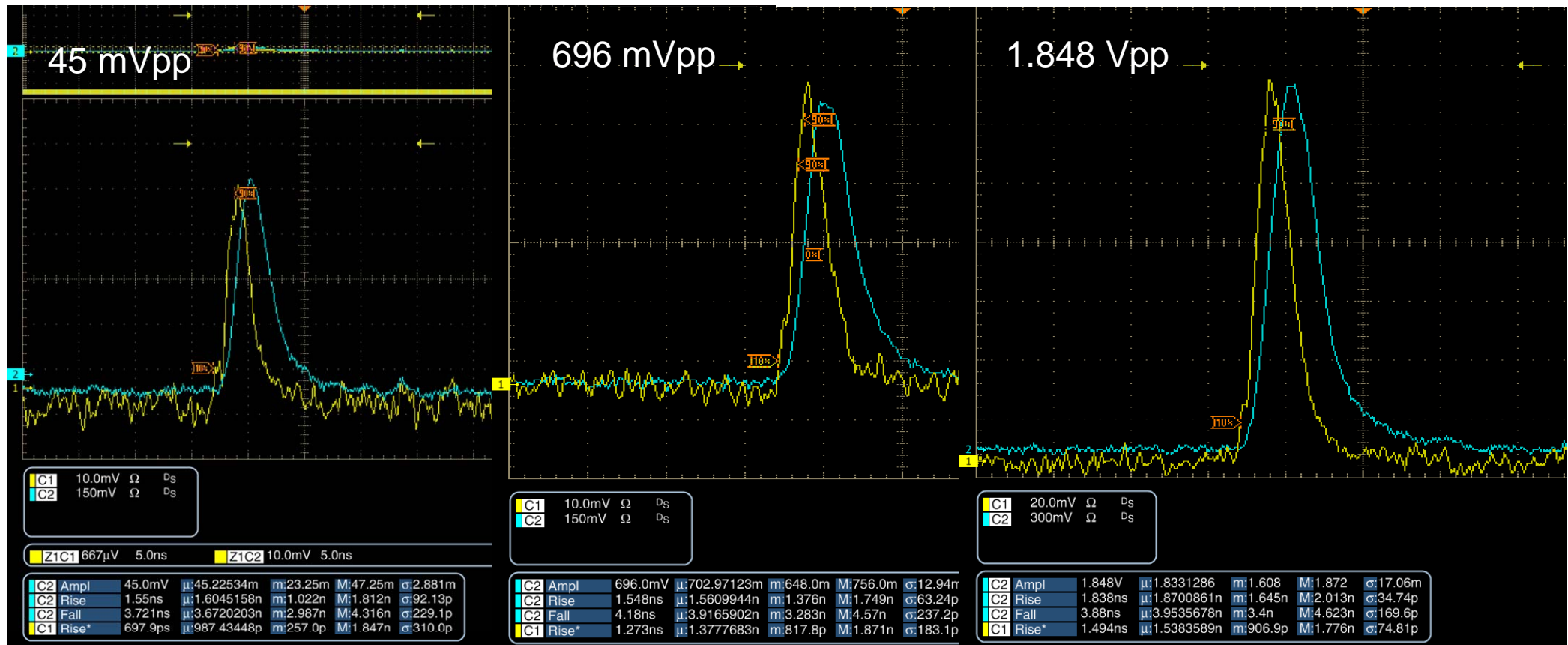
IV. ACTA3: pulse shape

- Good uniformity between small and large signal




 
IV. ACTA3: pulse shape

- Good uniformity between small and large signal



 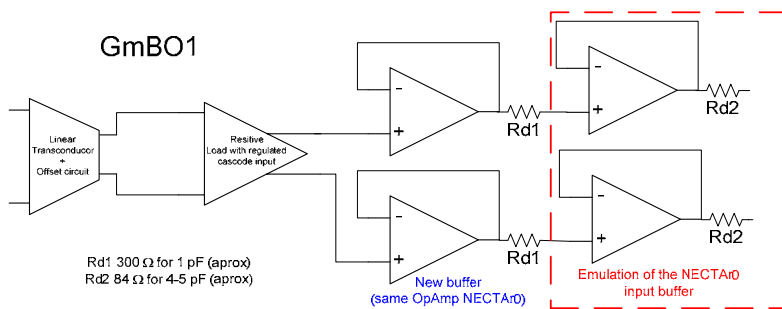
IV. ACTA3: frequency response

- BW of GmBO1 is even larger
 - Additional buffer !
- 300 MHz BW for ACTA3 + NECTARO input buffer
 - Need a very careful Rd tuning
 - BW vs stability
 - Environment more controlled
 - Same die
 - Postlayout simulation



 
IV. ACTA3: linearity

- Good linearity performance ($< 1\%$ for > 1 Vpp, $< 5\%$ up to 2 Vpp)
- Trade-off between linearity and power consumption



 
IV. ACTA3: Offset generation: GmBO5

- DC offset is controlled by the current "Ibof"




 
IV. ACTA3: Offset generation: transfer function

- Similar behaviour for G_mBO1 and G_mBOs1



 
 
IV. ACTA3: temperature compensation

- Controlling temperature dependence of the gain
 - Transconductor TC is about $-0.2\%/C$
 - Compensated by adjusting the TC of the current (I_{cf}) controlling floating voltage source
 - Final TC $\approx -0.05\%/C$ (1% for 20 C variation in one night)
- Band gap current reference (I_b) with TC $\approx +180\text{ ppm}/C$



  
IV. ACTA3: noise

- Channel thermal noise of the input differential pair dominates
 - Wideband amplifier: $1/f$ noise not relevant: use NMOS
 - Cross-coupling degrades noise performance: g_m subtraction
- For input referred series noise $< 3 \text{ nV}/\sqrt{\text{Hz}}$
 - $G_m > 5 \text{ mS}$: large $K (W)$ and/or bias offset V_b
 - Tradeoff between noise and large signal handling
- Noise increases with differential pair bias current



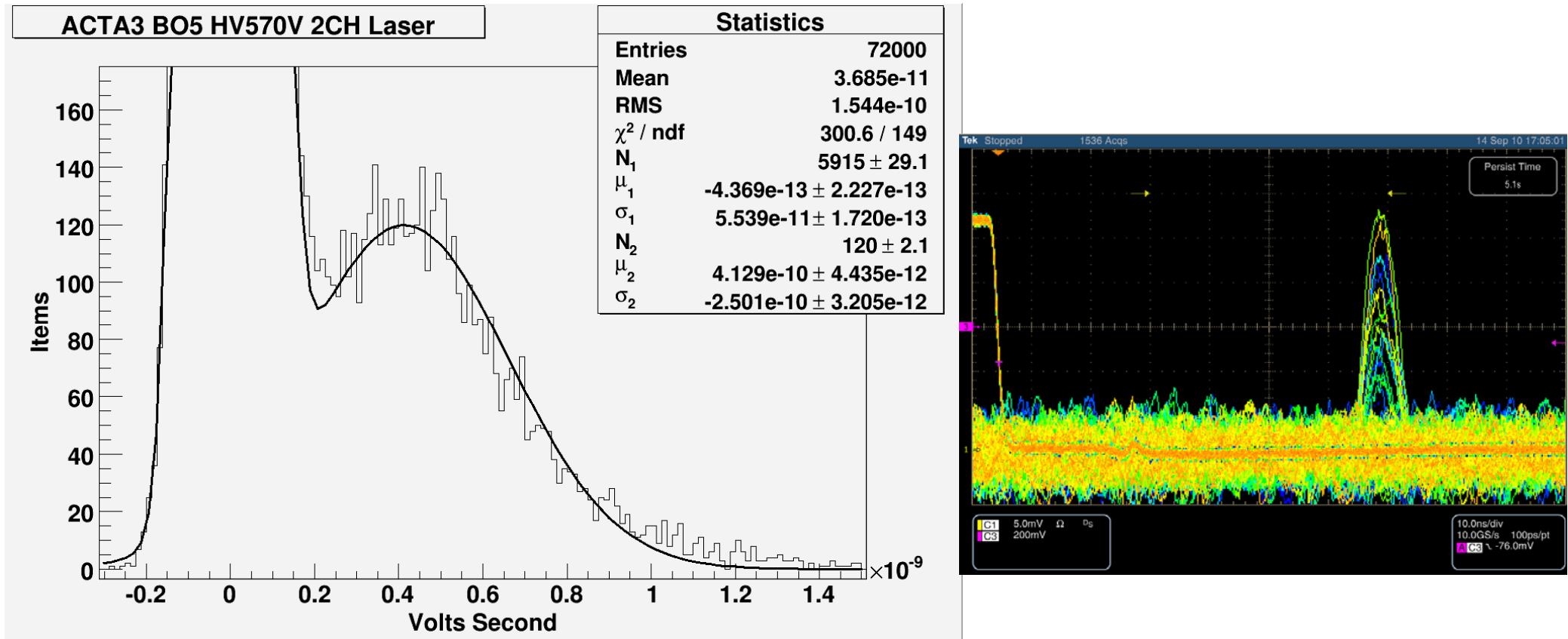IV. ACTA3: single photoelectron response

- Single photoelectron response at PM nominal gain ($2 \cdot 10^5$)
 - With R5900 PM, not optimal for SPE resolution
 - To be done with PM developed for CTA



Outlook

- I. Introduction
- II. The circuit
- III. First prototype: ACTA
- IV. Second prototype: ACTA3
- V. Summary**

V. Summary

- Alternative architecture for wideband pulse amplifiers
 - Gain up to 20
 - Bandwidth
 - > 400 MHz for $C_L < 1$ pF
 - > 300 MHz for $C_L < 5$ pF
 - Linearity $< 1\%$ for 1Vpp and $< 3\%$ for 2 Vpp
 - For fast “closed loop” amplifiers, linearity is usually limited by slew rate
- Intrinsic BW of the core amplifier (without buffer) > 600 MHz
 - BW > 1 GHz in 130 nm technology ?
- Highly tunnable
 - Gain
 - DC offset : ADC interface
 - Linearity vs power


*GBW > 6 GHz in
0.35 um CMOS
technology*



Thank you !


Linear amplifier: diff. pair with degeneration

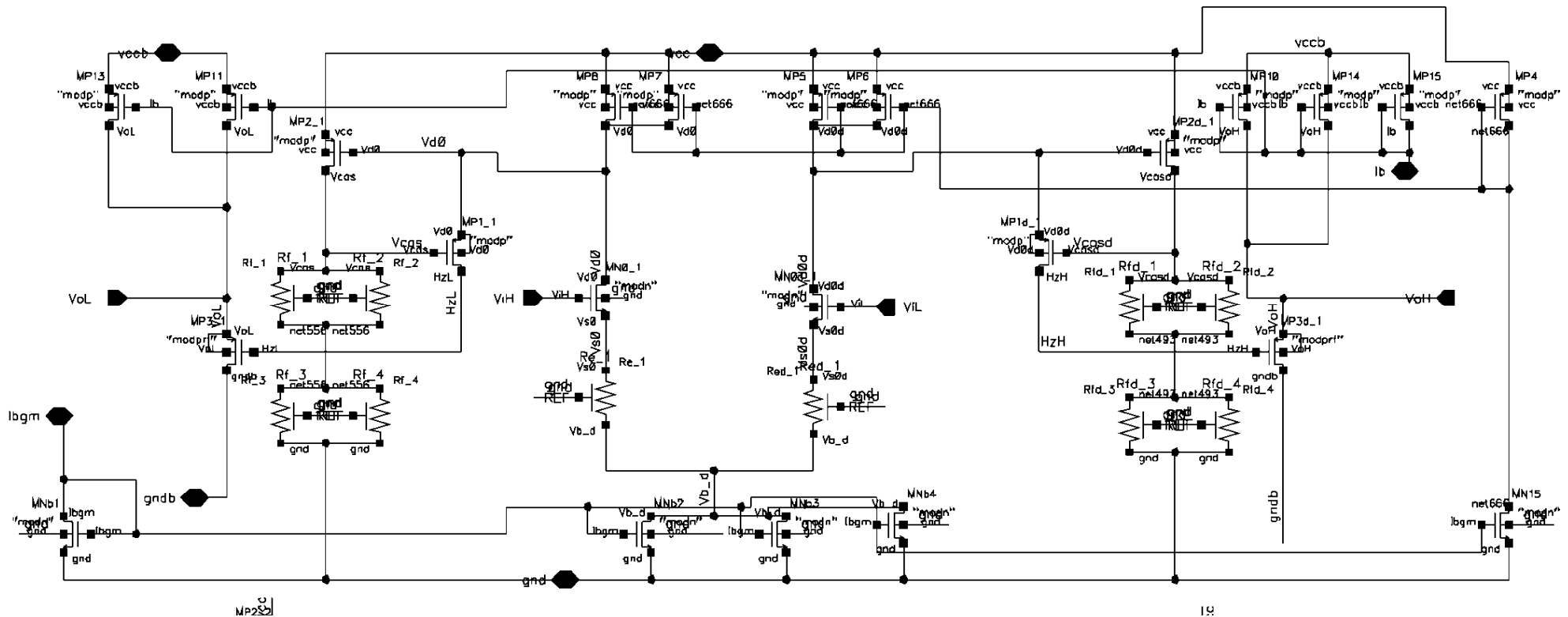- Three stages:
 - HF transconductor: source degenerated MOS diff. pair: V to I
 - Cascoded common gate amplifier: I to V
 - Source follower: low impedance driver (up to 3pF cap. load)
- Post-layout simulation: 5 GHz GBW and 3% lin error (VoD 1.7 V)




Results: linear amplifier: degenerated transistor

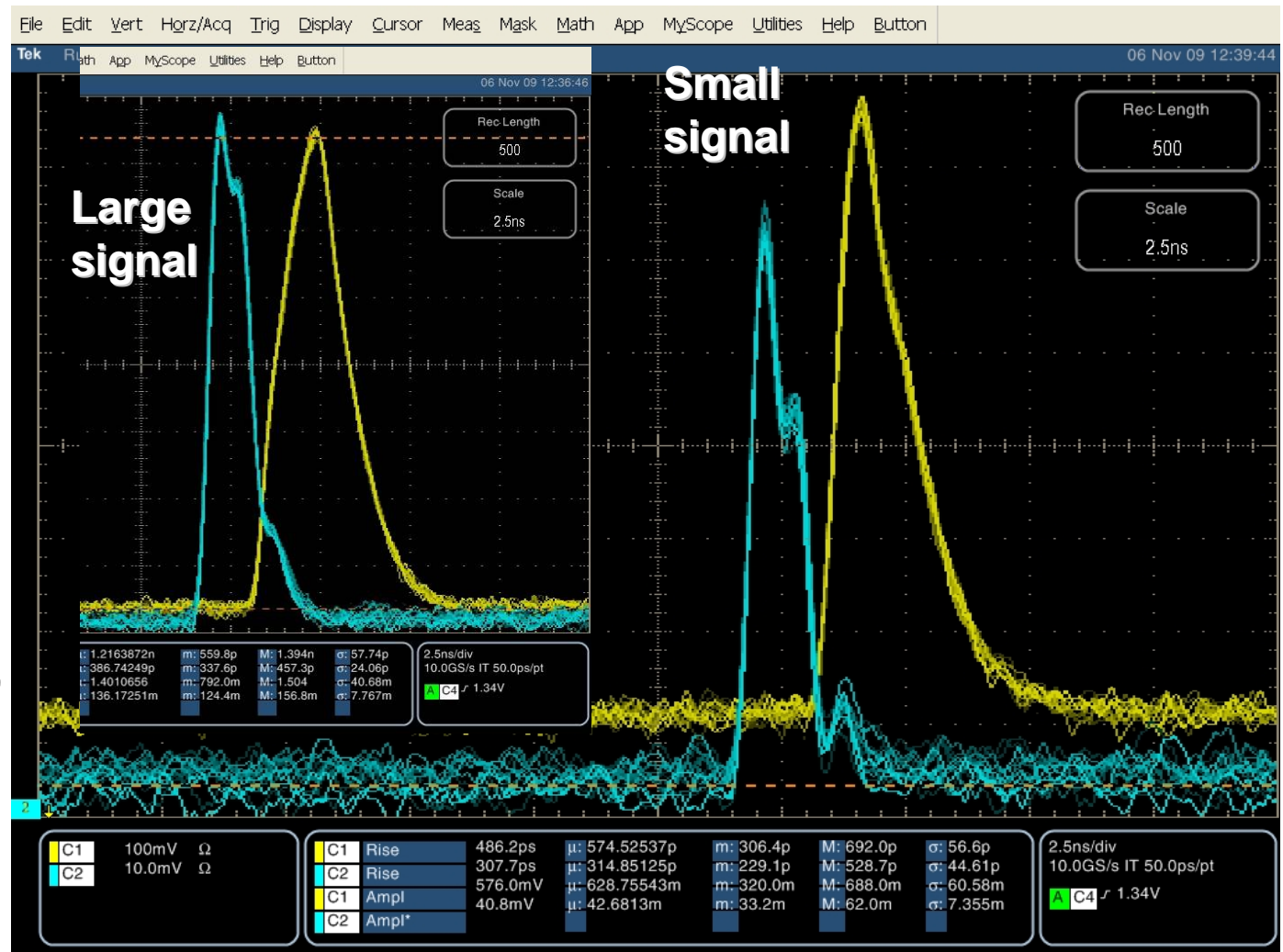- Working
 - Blue: input
 - Yellow: output
 - No ringing
- Fast input pulse
 - Rise: 300 ps
- Output pulse
 - Rise time:
 - Small signal ($< 1V$)
 - 574 ps
 - High signal ($> 1V$)
 - 1.2 ns





Preliminary results: linear amplifier: degenerated transconductor

 - **Gain**
 - About 13,5
 - Slightly tunnable
- **Linear range**
 - About 1.5 V



 
 
III. First prototype: test set-up

- Two test cards
 - General charact
 - Fast pulse generation
 - Bias current though stable ref
 - S-parameter
 - Minimal components
- Acquisition
 - Scope:
 - 1.7 GHz
 - 20 GS/s
 - Probe: diff. 4 GHz
- Test just started
 - < 1 week



I. Introduction: ACTA3


- **Second prototype (ACTA3)**
 - Better linearity
 - Low power output driver:
 - Class AB amplifier
 - New version of a SAM OpAmp
 - Collaboration with Eric
 - Temperature compensation
 - Control of DC offset as needed for ADC

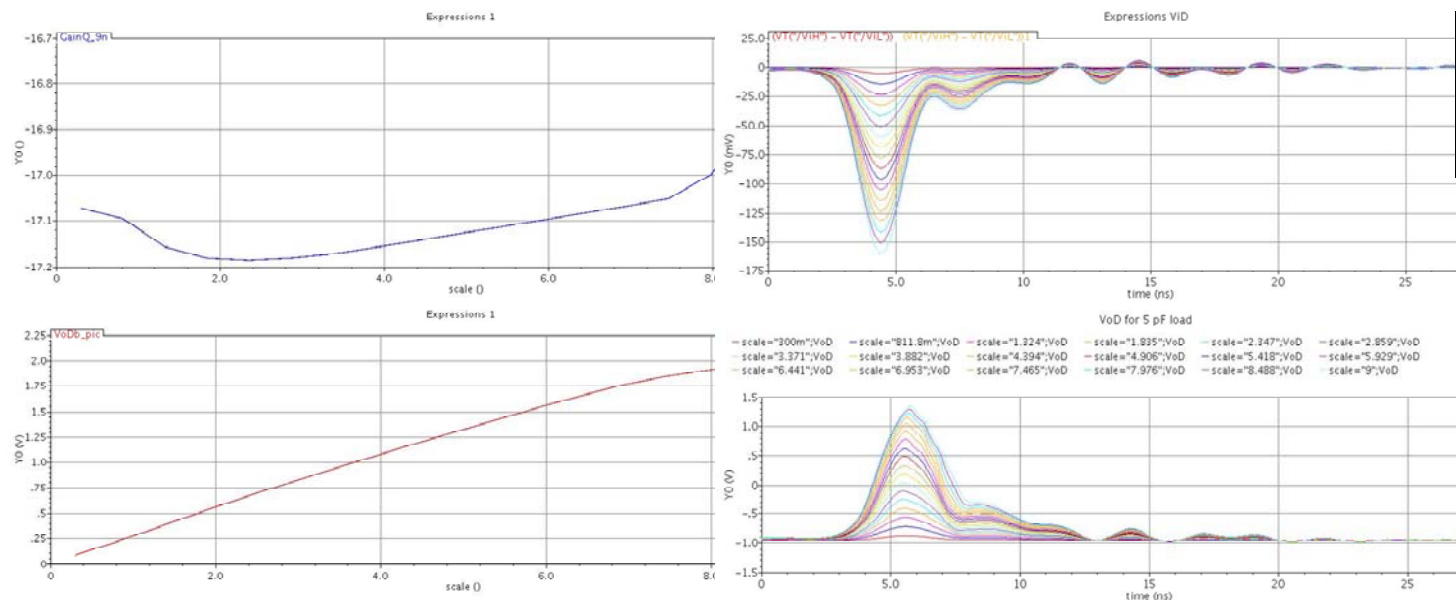 

CMOS 0.35um
AMS 3 mm²
Submitted: April 2010
Received: end July 2010

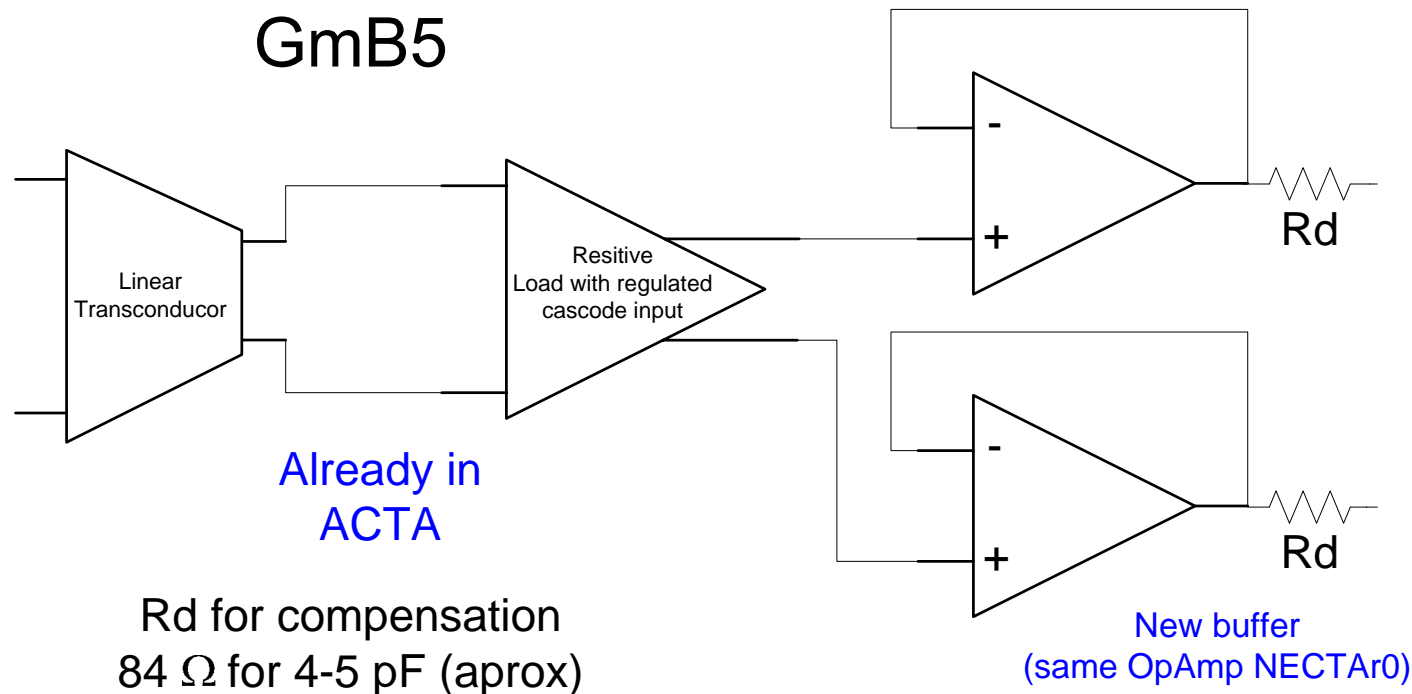
II. Blocks in ACTA3: GmB5

- Same gain block as in ACTA
- New buffer
 - Based on the same OpAmp used for NECTAR0 input buffers
 - Colaboration with Saclay
- Compensation resistor sized to drive output pads (4-5 pF load)
- Not tested for the moment, only to "debug"



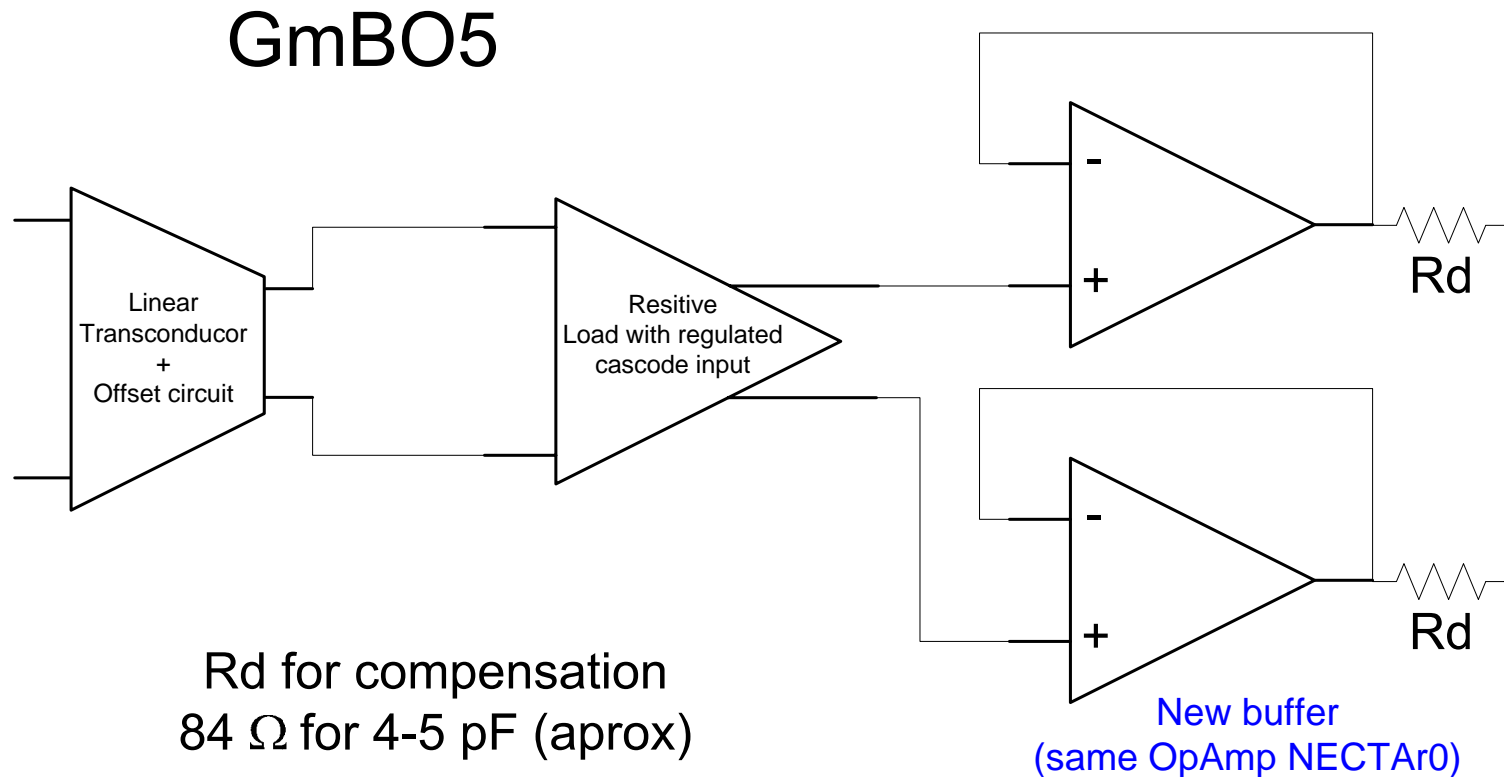
II. Blocks in ACTA3: GmBO5

- As GmB5 but gain stage is modified to generate the DC offset required by ADC
- Compensation resistor sized to drive output pads (4-5 pF load)



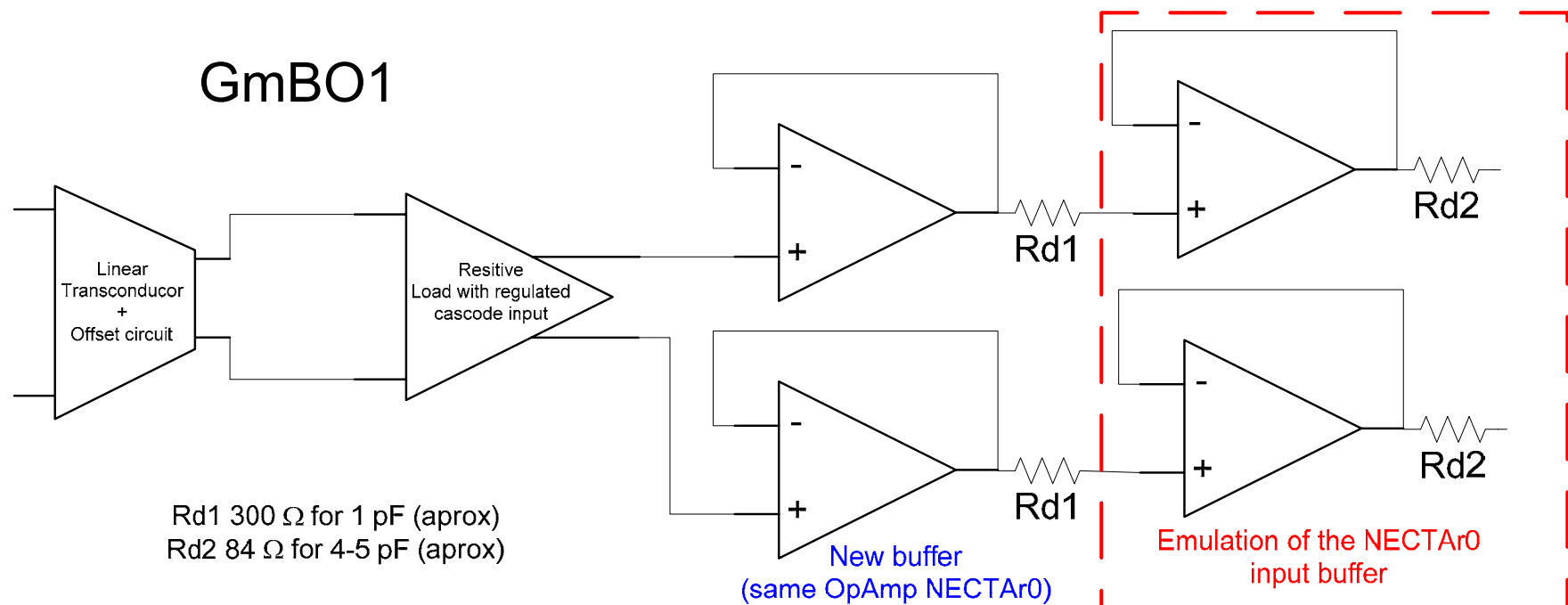
II. Blocks in ACTA3: GmBO1

- As GmBO5 but the amplifier (Rd1) is adjusted to drive a smaller capacitance:
 - It should be the case if it is integrated in the analogue memory chip
 - An additional buffer is added to emulate the NECTAr0 input stage and test the chain



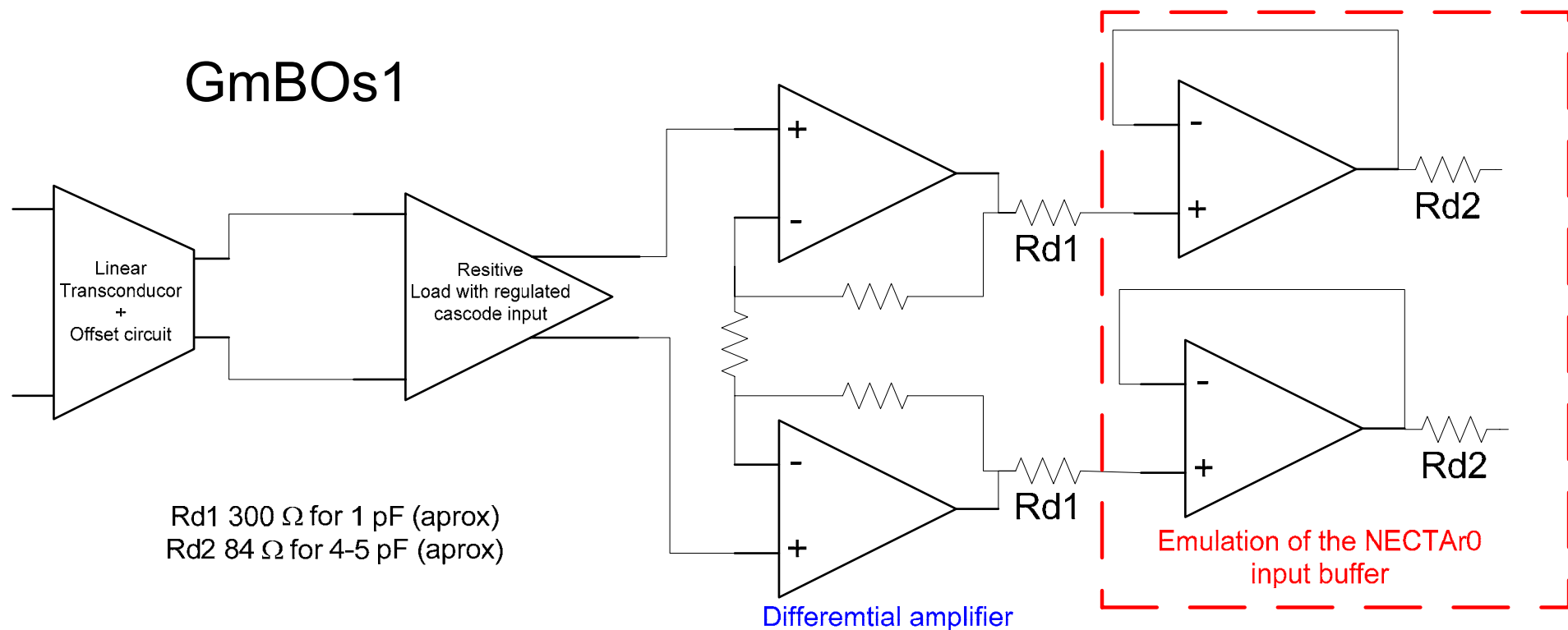
II. Blocks in ACTA3: GmBOs1

- As GmBO1 but the buffer is replaced by a fully differential amplifier:
 - Subtract common mode signals as soon as possible (CMRR, PSRR)



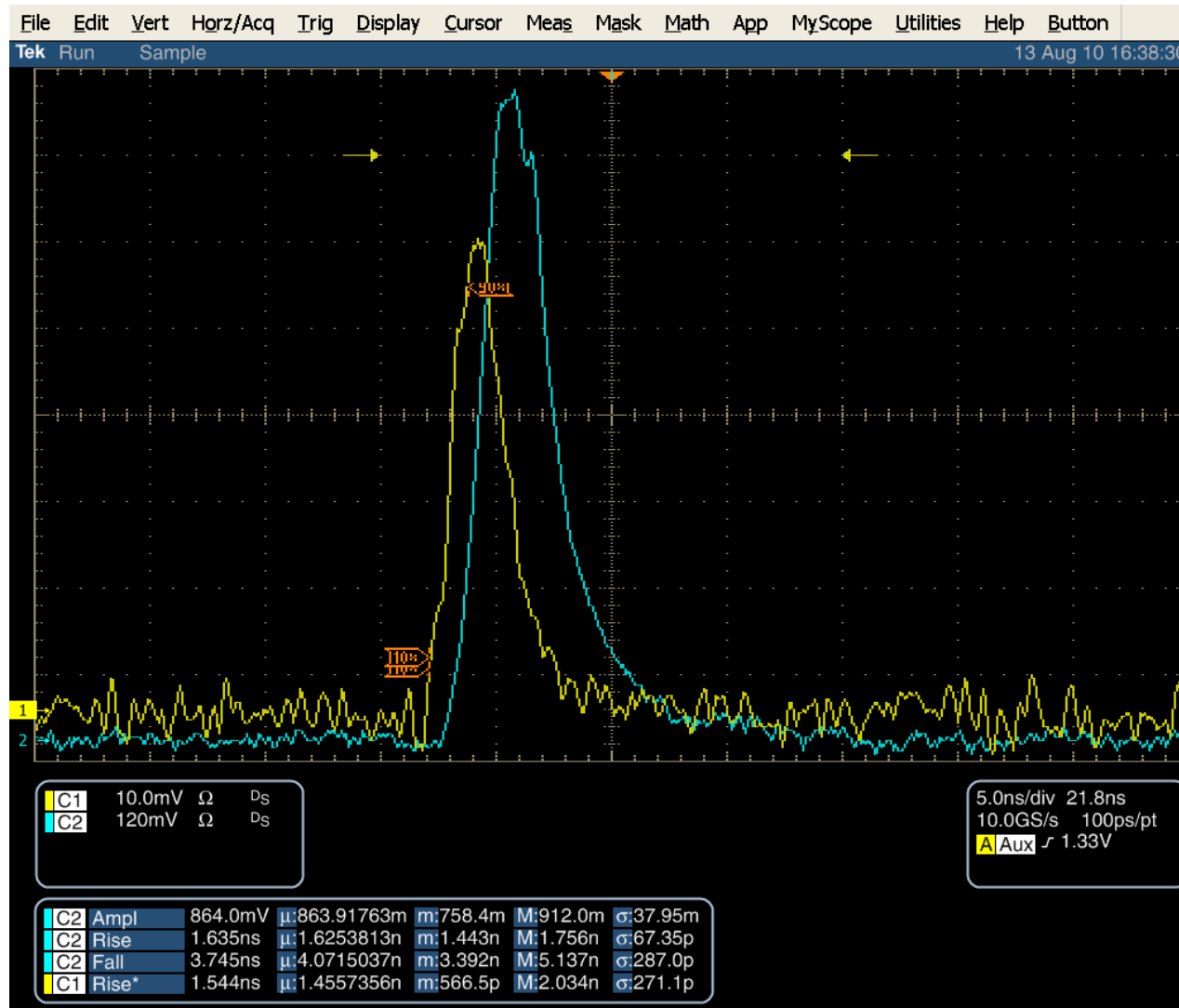
III. Pulse shape: GmBO1

- Second order response effects in the shape? (small...)



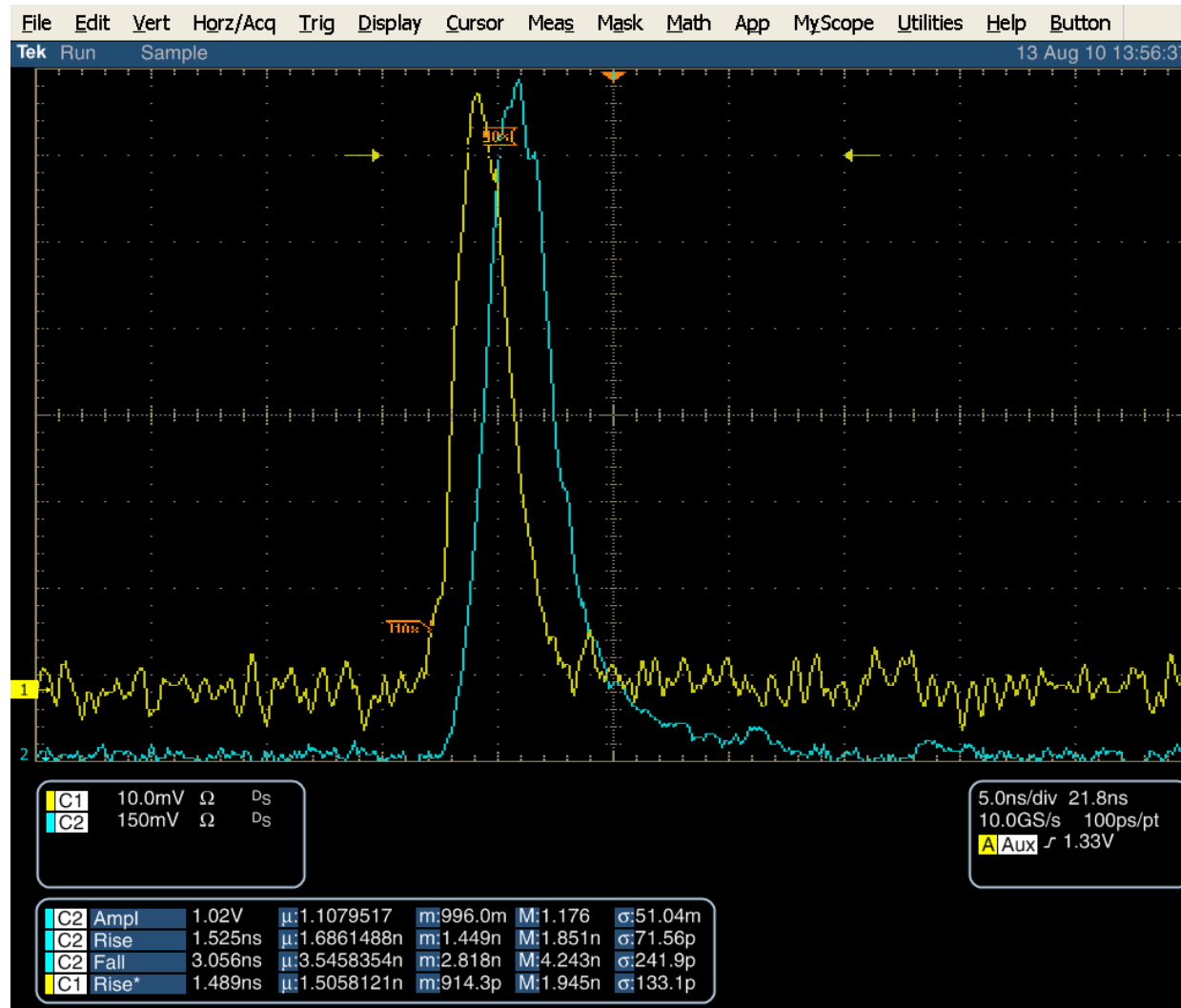
III. Pulse shape: GmBOs1

- Second order response effects in the shape? (small...)



 
IV. Behaviour of the new buffer: class B boost control

- A current control I_{bfol} has to be set to $> 30 \mu A$ to be sure that the class B current boost is off at the quiescent state



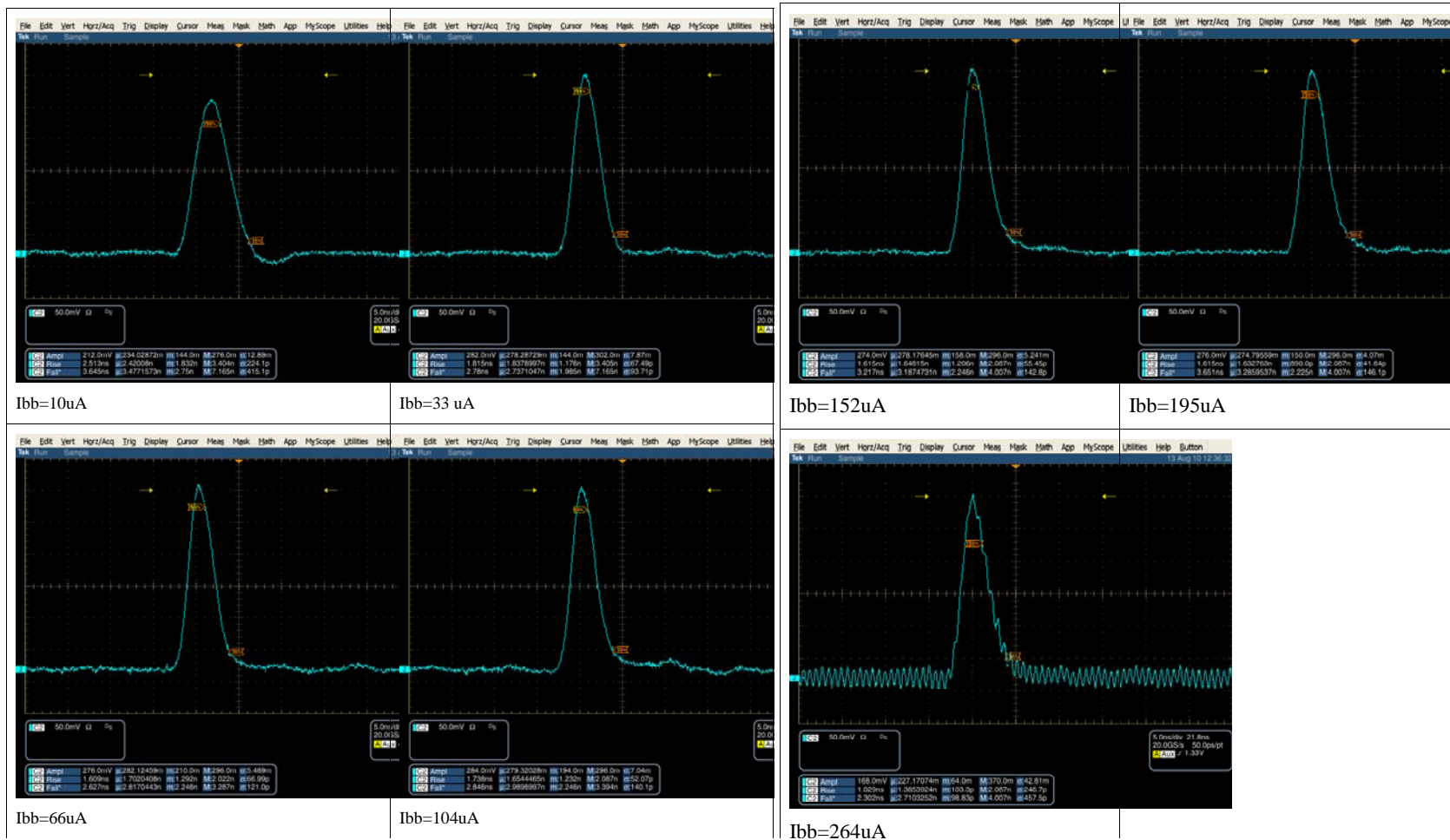
IV. Behaviour of the new buffer: bias current (buffer driving 5 pF)

- Bias current ($4 \cdot I_{bbpp}$):
 - If too low ($< 75\mu\text{A}$ for 5pF, $< 45\mu\text{A}$ for 1 pF) GBW is too low
 - If too high ($> 200\mu\text{A}$) phase margin too low




 
V. Bandwidth: GmBO5

- Nice first order response with little non-linearity up to 2 V, but...
- However BW is only 200 MHz
 - Rd was adjusted to have 300 MHz !!!
 - With an external Cload of 3 pF + extracted capacitances including pads



  
V. Bandwidth: GmBO5

- It seems that the BW is dominated by the pole $R_d \cdot C_{load}$
 - After some surgery it was possible to measure the BW with shorter PCB traces: increases to 250 MHz
 - The response looks like a first order response (up to 500 MHz)
- Possible explanation
 - External C_{load} is larger than expected
 - Process variation effects in R and C



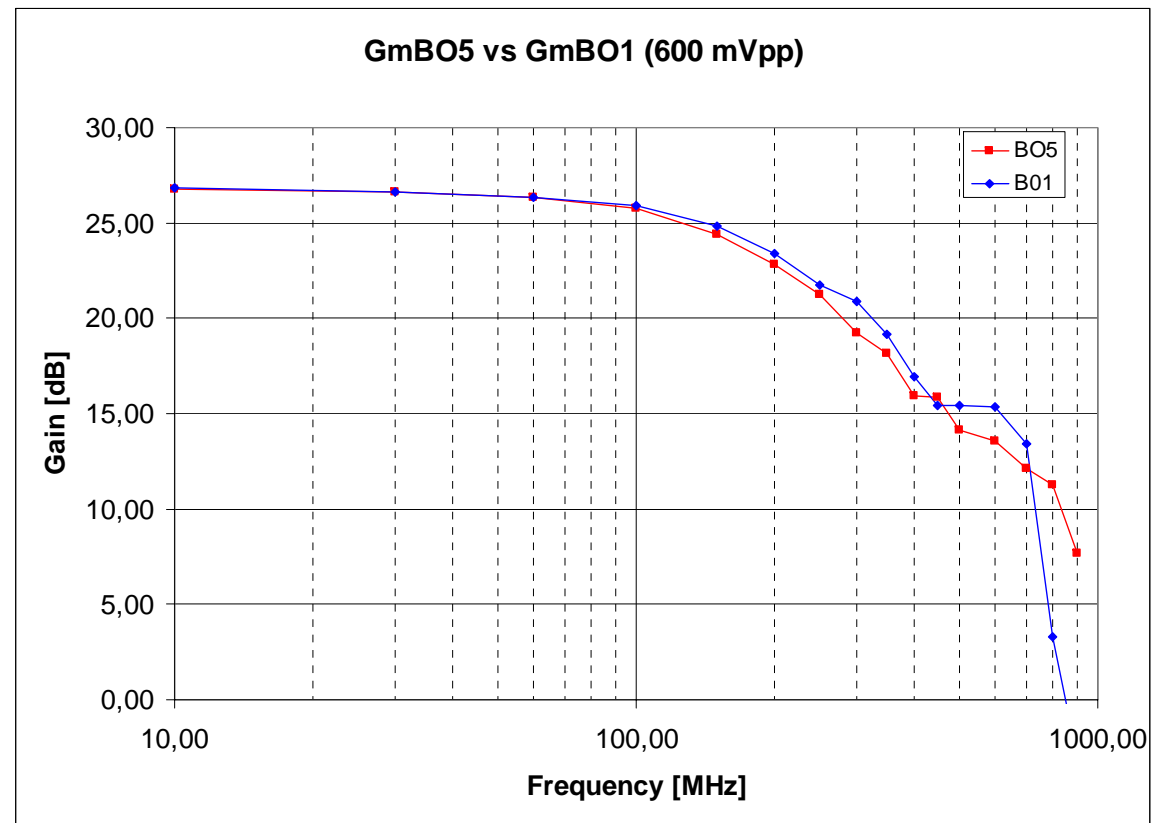
V. Bandwidth: GmBO5 vs GmBO1

- Additional confirmation that the BW is limited by the $R_d \cdot C_{load}$
 - The BW of GmBO1 is even larger
 - It has an additional buffer !
- Should be possible to achieve > 300 MHz BW for the full amplification
 - ACTA3 + NECTARO input buffer
 - Need a very careful tuning of R_d
 - BW vs stability
 - Environment more controlled
 - ACTA3 in NECTAR silicon
 - Postlayout simulation with Eric
- Side effect:
 - Underestimation of lin error ?
 - Seems to be enough margin...



 VI. Linearity


- Remember that gain depends on two bias current:
 - I_{bgm} : linearized transconductor differential pair tail current
 - I_{cf} : current controlling floating voltage supply current
- “Nominal” condition is $I_{bgm}=1500 \mu A$ and $I_{cf}=150 \mu A$ (pulse gain = 16, DC gain = 20)
- Results will be shown for this condition
- Tested for other conditions, results available for other conditions:
 - Trade-off consumption / linearty
 - Nominal consumption is 10 mA




VI. Linearity: GmB05

- Amplitude measurement
- Linearity residue:
 - < 1 % of the Full Scale (F.S.) for outputs < 1.3 Vpp
 - < 3 % F.S. for output < 1.6 Vpp

Guany


 


Error

 

  VI. Linearity: GmB05


- Charge (area) measurement
- Linearity residue:
 - < 1 % of the Full Scale (F.S.) for outputs < 1.3 Vpp
 - < 3 % F.S. for output < 1.6 Vpp



VI. Linearity: GmB01


- Similar to GmB05

Guany

 


Error

Amplitude

 

Error


Charge

 

VI. Linearity: GmB0s1

- Slightly worst
- Gain is 10 % higher

Guany


 


Error

Amplitude

Error

Charge

  

IV. ACTA3: Offset generation: effect on linearity and gain

- Linearity is ok at the gain plateau
- Optimal region around I_{bof} 300 μA

